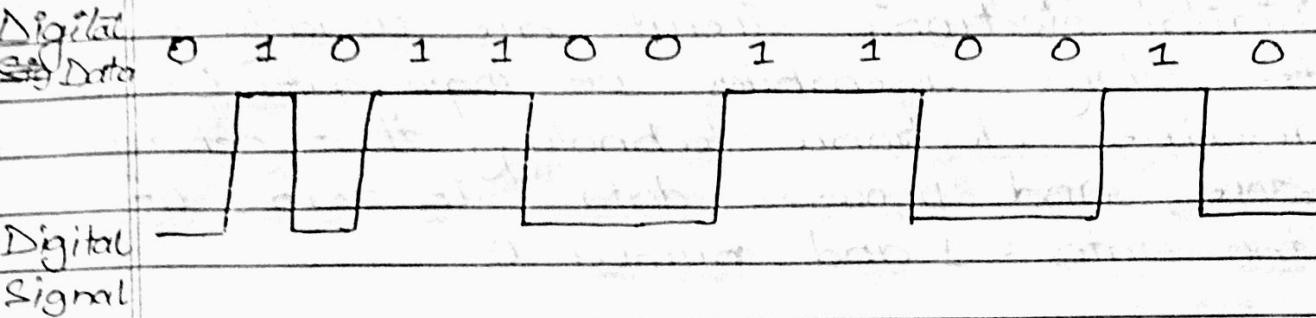


## Digital Electronics

### Digital Signal Representation



Digital signal is represented by in the form of square wave whereas analog is in the form of sine wave.

Sine waves are continuous in nature and square are discrete.

What is Digital Electronics?


- Digital Electronics deals with the electronic manipulation of numbers, or with the manipulation of varying quantities by means of numbers. Because it is convenient to do so, today's digital systems deal only with the numbers "zero" and "one", because they can be represented easily by "off" and "on" within a circuit.
- Digital stand for digit, digital electronics basically has two conditions which are possible, 0 (low logic) and 1 (high logic). Digital electronic systems use a digital signal that are composed of mathematical features to work.

- 1 as true and 0 as false are called bit and the group of bits are named byte.
- Digital electronic circuits are usually made from large assemblies of logic gates. Digital describes electronic technology that generates, stores, and processes data in terms of two states: 1 and number 0.

### Analog vs Digital

Many systems use a maximum of analog and digital electronics to take advantage of each technology.

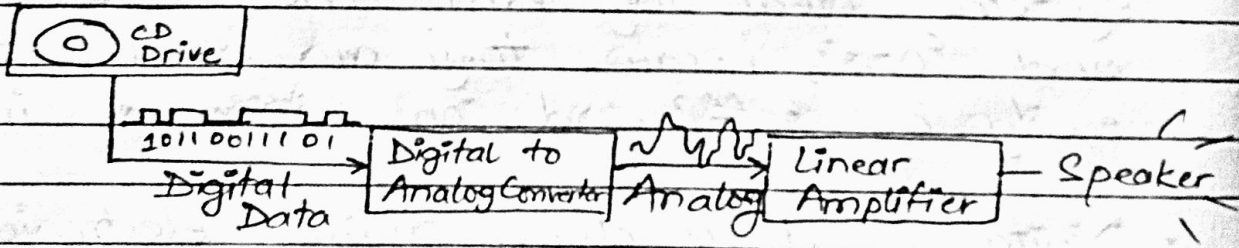Example: A typical CD player accepts digital data from the CD drive and converts it to an analog signal for amplification. Digital data CD drive 10110011101 Analog reproduction of music audio signal speaker sound waves digital-to-analog converter linear amplifier




⇒ Digital data is in the form of 0 and 1 and can be understood by computer only whereas analog data cannot be understood by computer.




Amplifier → to increase the strength of signal.


### Analog signal representation

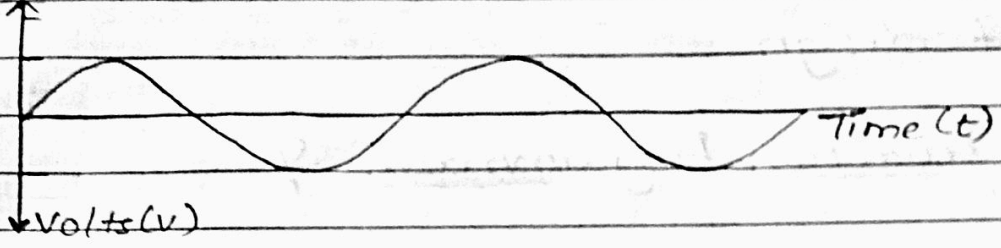

### Digital signal representation

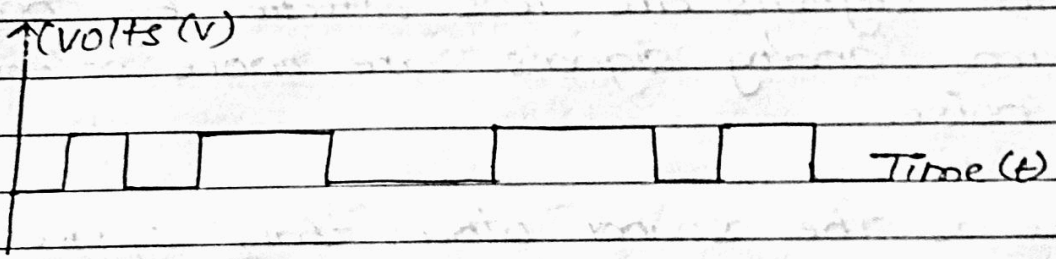
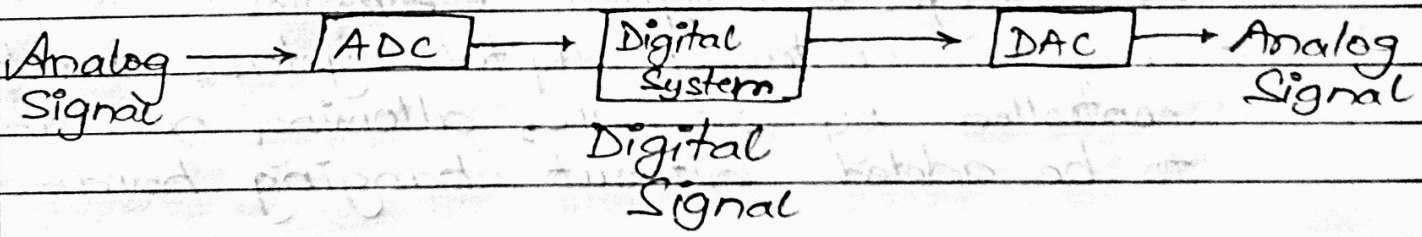
### Conversion of Analog to Digital Signal



There are two types of converters:-

1. ADC → Analog to Digital Converter
2. DAC → Digital to Analog converter

## Benefits of Digital over Analog

- Reproducibility

- Not effected by noise means quality

- Ease of design

- Data Protection Programmable Speed

- Economy

⇒ ~~Data~~

⇒ Digital signals are less affected by noise whereas analog signals are more affected by noise.

⇒ Noise is the sound other than square or sine waves.

## Advantages of Digital Electronics

- Computer controlled digital systems can be controlled by software, allowing new functions to be added without changing hardware

- Information storage can be easier in digital systems than in analog ones.

- The noise immunity of digital systems permits data to be stored and retrieved without noise.

- In a digital system are easier to design and more precise representation of a signal can be obtained by using more binary digits to represent it.
- More digit circuitary can be fabricated on IC chips.
- Error management method can be inserted into the signal path. To detect errors, and then correct the errors, or at least ask for a new copy of the data.

### Disadvantages of Digital Electronics

- Conversion to digital format and re-conversion to analog format is needed, which always include the loss of information.
- In some cases, digital circuits use more energy than analog circuits and produce more heat and need heat sinks.
- Digital circuits are sometimes more expensive, especially in small quantities.



## Applications of Digital Electronics


Its applications are infinite, ~~enjoying~~ ranging for high end computing to miniature circuits that can be very versatile, signal processing, communication, etc. Digital electronics is currently rapidly developing and removing conventional analogue machines due to its high speed, more accuracy and greater flexibility.

\* The digital system send the data in the form of packets of digital codes, thus we can encode and decode them in various formats and codes.

\* Data encryption is also possible in the digital systems, hence data transmission is more secure and can be manipulated in many formats.

\* Digital systems are much advantageous in communications Data Transmission using Digital Systems

## Number System

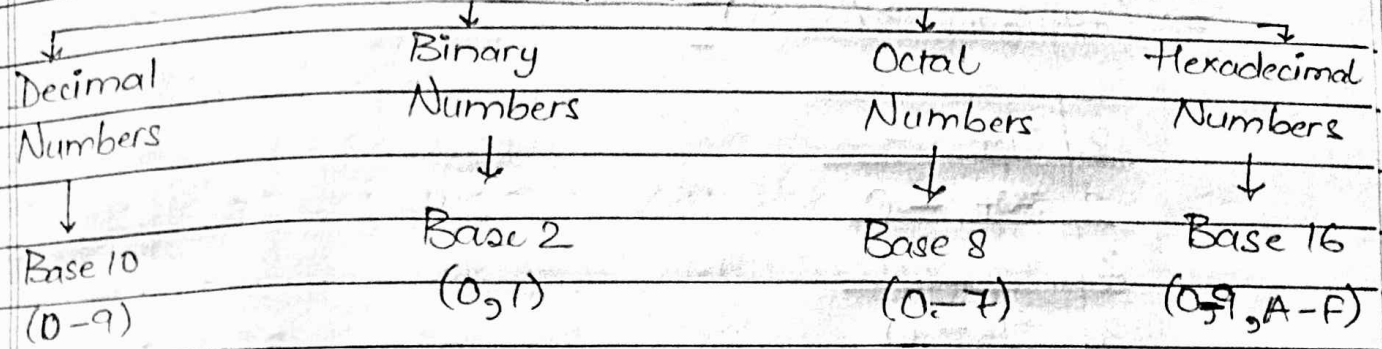

Number system	Base (Radix)	Digits	Example
Binary	2	0, 1	$(1011, 11)_2$
Decimal	10	0, 1, 2, 3, 4, 5, 6, 7, 8, 9	$(3567.29)_{10}$
Octal	8	0, 1, 2, 3, 4, 5, 6, 7	$(356.11)_8$
Hexadecimal	16	0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F (A=10, B=11, C=12, D=13, E=14, F=15)	$(ABC.13)_{16}$

Conversions ↓

$\Rightarrow (74)_{10} \rightarrow ( \quad )_2$

2	74
2	37 - 0
2	18 - 1
2	9 - 0
2	4 - 1
2	2 - 0
2	1 - 0
	0 - 1

$(74)_{10} \rightarrow (1001010)_2$

$\Rightarrow (74.04)_{10} \rightarrow ( \quad )_2$

2	74		
2	37 - 0	$0.4 \times 2 = 0.08$	0
2	18 - 1	$0.08 \times 2 = 0.16$	0
2	9 - 0	$0.16 \times 2 = 0.32$	0
2	4 - 1		
2	2 - 0		
2	1 - 0		
	0 - 1		

$(74.04)_{10} \rightarrow (1001010.000)_2$



$\Rightarrow (242.4)_{10} \rightarrow ( \quad )_2$

2	242		
2	121	-0	
2	60	-1	$0.4 \times 2 = 0.8$
2	30	-0	$0.8 \times 2 = 1.6$
2	15	-0	$0.6 \times 2 = 1.2$
2	7	-1	
2	3	-1	
2	1	-1	
	0	-1	

$(242.4)_{10} \rightarrow (11110010.011)_2$

$\Rightarrow (73.04)_{10} \rightarrow ( \quad )_8$

8	73		$0.04 \times 8 = 0.32$	0
8	9	-1	$0.32 \times 8 = 2.56$	2
8	1	-1	$0.56 \times 8 = 4.48$	4
	0	-1		

$(73.04)_{10} \rightarrow (111.024)_8$

$\Rightarrow (73.04)_{10} \rightarrow ( \quad )_{16}$

16	73		$0.04 \times 16 = 0.64$	0
16	4	-9	$0.64 \times 16 = 10.24$	10 $\rightarrow$ A
	0	-4	$0.24 \times 16 = 3.84$	3

$(73.04)_{10} \rightarrow (49.0A3)_{16}$

$\Rightarrow (743.02)_{10} \rightarrow ( )_2$

2	743			
2	371	-1		
2	185	-1	$0.02 \times 2 = 0.04$	0
2	92	-1	$0.04 \times 2 = 0.08$	0
2	46	-0	$0.08 \times 2 = 0.16$	0
2	23	-0	$0.16 \times 2 = 0.32$	0
2	11	-1		
2	5	-1		
2	2	-1		
2	1	-0		
	0	-1		

$(743.02)_{10} \rightarrow (1011100111.000)_2$

$\Rightarrow (243.1)_{10} \rightarrow ( )_2$

2	243			
2	121	-1		
2	60	-1	$0.1 \times 2 = 0.2$	0
2	30	-0	$0.2 \times 2 = 0.4$	0
2	15	-0	$0.4 \times 2 = 0.8$	0
2	7	-1		
2	3	-1		
2	1	-1		
	0	-1		

$(243.1)_{10} \rightarrow (11110011.000)_2$

$$\Rightarrow (742.04)_{10} \longrightarrow ( )_8$$

8	742		
8	92 - 6	<del><math>0.4 \times 8 = 3.2</math></del>	<del>3</del>
8	11 - 4	$0.2 \times 8 = 1.6$	
8	1 - 3		
	0 - 1		
		$0.04 \times 8 = 0.32$	0
		$0.32 \times 8 = 2.56$	2
		$0.56 \times 8 = 4.48$	4

$$(742.04)_{10} \longrightarrow (1346.024)_8$$

$$\Rightarrow (745)_{10} \longrightarrow ( )_{16}$$

16	745
16	46 - 9
16	2 - 14
	0 - 2

$$(745)_{10} \longrightarrow (2E9)_{16}$$




$\Rightarrow (748.3)_{10} \rightarrow (\quad)_{16}$

16	748		
16	46 - 12	$0.3 \times 16 = 4.8$	4
16	2 - 14	$0.8 \times 16 = 12.8$	12
	0 - 2		

$(748.3)_{10} \rightarrow (2EC.4C)_{16}$


## Logic Gates and Boolean Algebra

### Logic Gates

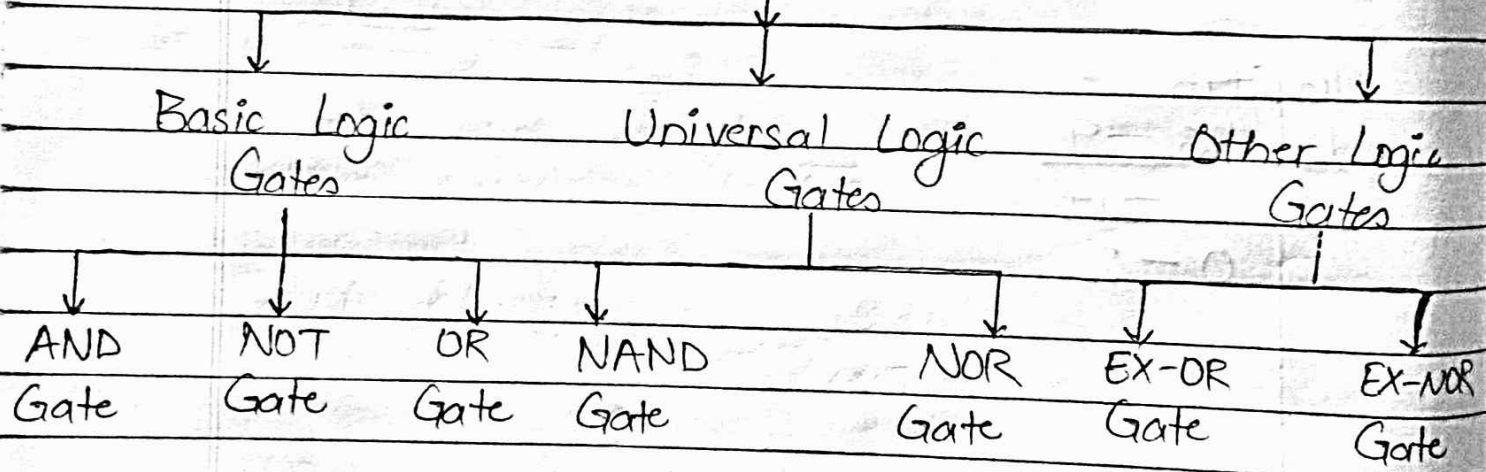

$\Rightarrow$  NAND Gate and NOR Gate are called universal logic gates because any gate can be made with the help of these two logic gates.

### AND Logic Gate

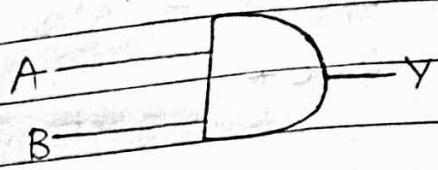


integrated circuit  
TC no. for AND Gate  
↓  
7408

Boolean expression:  $Y = A \cdot B$

### Truth Table ↓

A(input)	B(input)	Y(output)
0	0	0
0	1	0
1	0	0
1	1	1

### OR Logic Gate

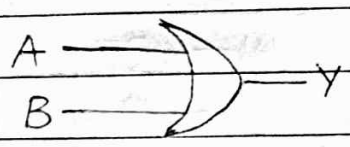

TC no. for OR Gate  
↓  
7432

Boolean Expression:  $Y = A + B$

### Truth Table ↓

A(input)	B(input)	Y(output)
0	0	0
0	1	1
1	0	1
1	1	1

### NOT Logic Gate



IC no. for NOT Gate  
↓  
7404

Boolean expression  $Y = \bar{A}$

Truth Table ↓

A (input)	Y (output)
0	1
1	0

### NAND Logic Gate



IC no. for NAND Gate  
↓  
7400



Boolean expression  $Y = \overline{A \cdot B}$


Truth Table ↓

A (input)	B (input)	Y (output)
0	0	1
0	1	1
1	0	1
1	1	0




### NOR Logic Gate

IC no. for NOR Gate

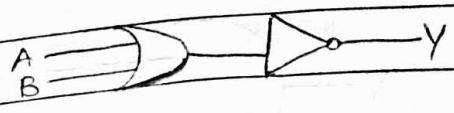

↓  
7402

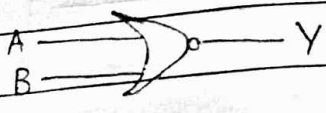


Boolean expression  $Y = \overline{A+B}$

Truth Table ↓

A(input)	B(input)	Y(output)
0	0	1
0	1	0
1	0	0
1	1	0

### EX-OR Logic Gate

IC no. for XOR Gate

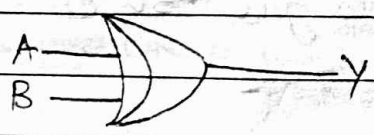


↓  
7486

Boolean Expression  $Y = A \oplus B \rightarrow \bar{A}B + A\bar{B}$

Truth Table ↓

A(input)	B(input)	Y(output)
0	0	0
0	1	1
1	0	1
1	1	0

## EX-NOR Logic Gate

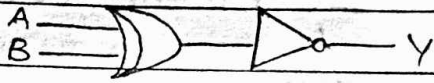

Boolean expression  $Y = \overline{A \oplus B} = \overline{\overline{A}B + A\overline{B}}$

Truth Table

A(input)	B(input)	Y(output)
0	0	1
0	1	0
1	0	0
1	1	1

⇒ TC of all the gates are 14 pins IC

To activate any TC, you need to give +5V on 14<sup>th</sup> pin and 0V on 7<sup>th</sup> pin  
 ↓  
 Ground

⇒ In one TC of AND Gate, there are 4 AND Gates

We can calculate this as

Total pins = 14

Pins for power supply = 2

Pins left = 12

Pins in one AND Gate = 3

Total AND Gates in 1 IC =  $12/3 = 4$

⇒ Output for will be on 3, 6, 8, 11 for OR, AND, NAND, XOR, XNOR Gate.

⇒ Output will be on 2, 4, 6, 8, 10, 12 for NOT Gate.

⇒ Output will be on 1, 4, 10, 13 for NOR Gate

Conversions ↓

⇒  $(010.10)_2 \rightarrow ( )_{10}$

$$\begin{array}{cccc} 0 & 1 & 0 & . & 1 & 0 \\ 2^2 & 2^1 & 2^0 & & 2^{-1} & 2^{-2} \\ \hline & 2 & & & 0.5 & 0.25 \end{array}$$

$$0 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 + 1 \times 2^{-1} + 0 \times 2^{-2} = 0 + 2 + 0 + 0.5 + 0 = 2.5$$

$(010.10)_2 \rightarrow (2.5)_{10}$

⇒  $(0100.101)_2 \rightarrow ( )_{10}$

$$\begin{array}{ccccccc} 0 & 1 & 0 & 0 & . & 1 & 0 & 1 \\ 2^3 & 2^2 & 2^1 & 2^0 & & 2^{-1} & 2^{-2} & 2^{-3} \end{array}$$

$$4 + 0.5 + 0.125 = 4.625$$

$(0100.101)_2 \rightarrow (4.625)_{10}$

⇒  $(0100.100)_2 \rightarrow (4.5)_{10}$

⇒  $(0100.100)_8 \rightarrow ( )_{10}$

$$\begin{array}{ccccccc} 0 & 1 & 0 & 0 & . & 1 & 0 & 0 \\ 8^3 & 8^2 & 8^1 & 8^0 & & 8^{-1} & 8^{-2} & 8^{-3} \end{array}$$

$$164 + 0.125 = 16.125$$

$(0100.100)_8 \rightarrow (16.125)_{10}$



$$\Rightarrow (01010.101)_2 \rightarrow ( )_{10}$$

$$01010.101$$

$$2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0 \ 2^{-1} \ 2^{-2} \ 2^{-3}$$

$$8 + 2 + 0.5 + 0.125 = 10.625$$

$$(01010.101)_2 \rightarrow (10.625)_{10}$$

$$\Rightarrow (467.1)_8 \rightarrow ( )_2$$

$$(467.1)_8 \rightarrow (100110111.001)_2$$

8421  
0110  
100  
110

$$\Rightarrow (467.1)_{16} \rightarrow ( )_2$$

$$(467.1)_{16} \rightarrow (010001100111.00001)_2$$

$$\Rightarrow (010010110.101011)_2 \rightarrow ( )_8$$

8421  
010  
110  
101  
011

$$(010010110.101011)_2 \rightarrow (226.53)_8$$

$$\Rightarrow (010010110.101011)_2 \rightarrow ( )_{16}$$

8421  
1001  
0110  
1010  
1100

$$(010010110.101011)_2 \rightarrow (96.AC)_{16}$$

$$\Rightarrow (01001001.001011)_2 \rightarrow ( )_{16}$$

$$(010010101.001011)_2 \rightarrow (695.2C)_{16}$$

8421  
1001  
0101  
0010  
1100



$$\Rightarrow (74A.A5)_{16} \rightarrow ( )_8$$

8 4 2 1  
0 1 1  
1 0 1  
0 0 1  
0 1 0  
1 0 1  
0 0 1  
0 1 0

$$(74A.A5)_{16} \rightarrow (011101001010.10100101)_2$$

$$(011101001010.10100101)_2 \rightarrow (3512.512)_8$$

$$\Rightarrow (742.10)_8 \rightarrow ( )_{16}$$

8 4 2 1

$$(742.10)_8 \rightarrow (111100010.0010)_2$$

$$(111100010.0010)_2 \rightarrow (1E2.20)_{16}$$

$$\Rightarrow (ABC.9A)_{16} \rightarrow ( )_8$$

8 4 2 1  
1 0 1  
0 1 0  
1 1 1  
1 0 0  
1 1 0  
1 0 0

$$(ABC.9A)_{16} \rightarrow (101010111100.10011010)_2$$

$$(101010111100.10011010)_2 \rightarrow (5274.464)_8$$

# Binary Arithmetic

## Binary Addition ↓

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\begin{array}{r}
 1 \quad 1 \quad 1 \\
 011010 \\
 + 110101 \\
 \hline
 100101
 \end{array}$$

$$\begin{array}{r}
 111 \\
 1111 \\
 + 1101 \\
 \hline
 11010
 \end{array}$$

$$\begin{array}{r}
 1111 \\
 10111 \\
 + 01101 \\
 \hline
 100100
 \end{array}$$

## Binary subtraction ↓

A	B	difference	borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\begin{array}{r} 0^0 \text{ } 1^1 \\ \cancel{0} \text{ } \textcircled{0} \text{ } 11 \\ - 0100 \\ \hline 0111 \end{array}$$

$$\begin{array}{r} 0^0 \text{ } 1^1 \text{ } 0^0 \text{ } 1^1 \\ \cancel{0} \text{ } \cancel{0} \text{ } \textcircled{0} \text{ } 011 \\ - 0100100 \\ \hline 0101111 \end{array}$$

$$\begin{array}{r} 0^0 \text{ } 1^1 \text{ } 0^0 \text{ } 1^1 \text{ } 0^0 \text{ } 1^1 \\ \cancel{0} \text{ } \cancel{0} \text{ } \textcircled{0} \text{ } \textcircled{0} \text{ } 11 \\ - 0010101 \\ \hline 0011010 \end{array}$$

$$\begin{array}{r} 0^0 \text{ } 1^1 \text{ } 0^0 \text{ } 1^1 \text{ } 0^0 \text{ } 1^1 \\ \cancel{0} \text{ } \cancel{0} \text{ } \textcircled{0} \text{ } 1010 \\ - 0011001 \\ \hline 010001 \end{array}$$

$$\begin{array}{r} 0^0 \text{ } 1^1 \text{ } 0^0 \text{ } 1^1 \text{ } 0^0 \text{ } 1^1 \\ \cancel{0} \text{ } \cancel{0} \text{ } \cancel{0} \text{ } \textcircled{0} \text{ } 01 \\ - 000010 \\ \hline 011111 \end{array}$$

# Binary Multiplication

$$\begin{array}{r}
 1001 \\
 \times 10 \\
 \hline
 0006 \\
 1001x \\
 \hline
 10010
 \end{array}$$

$$\begin{array}{r}
 1111 \\
 \times 1111 \\
 \hline
 1111 \\
 1111 \\
 1111 \\
 1111 \\
 \hline
 11100001
 \end{array}$$

$$\begin{array}{r}
 1011 \\
 \times 0111 \\
 \hline
 1011 \\
 1011x \\
 1011xx \\
 0000xxx \\
 \hline
 1001101
 \end{array}$$

$$\begin{array}{r}
 01011 \\
 \times 1010011 \\
 \hline
 0100100 \\
 0101111
 \end{array}$$



## Boolean Algebra

⇒ Boolean Algebra is basically used to reduce the expression

### Laws of Boolean Algebra

NOT  $\bar{\bar{A}} = A$

AND  $A \cdot \bar{A} = 0$

$$A \cdot A = A$$

$$A \cdot 0 = 0$$

OR  $A + 0 = A$

$$A + \bar{A} = 1$$

$$A + 1 = 1$$

$$A + A + A = A$$

$$AB + A\bar{B}$$

$$= A(B + \bar{B}) = A$$

$$\because B + \bar{B} = 1$$

$$\bar{A}\bar{B} + A\bar{B}\bar{C} + ABC$$

$$\bar{A}\bar{B} + A\bar{B}(\bar{C} + C)$$

$$\because C + \bar{C} = 1$$

$$\bar{A}\bar{B} + A\bar{B}$$

$$= \bar{A}\bar{B} + A\bar{B}$$

$$\because \bar{B} + B = 1$$

$$= \bar{A}\bar{B} + A\bar{B}$$

$$(A+B)(A+C)$$

$$AA + AC + BA + BC$$

$$\because A \cdot A = A$$

$$A + AC + AB + BC$$

$$A(1+C) + AB + BC$$

$$\because 1+C=1$$

$$\begin{aligned}
 &A + AB + BC \\
 &A(1+B) + BC \quad \because 1+B=1 \\
 &= A + BC
 \end{aligned}$$

⇒ Distributive Theorem

$$(A+B)(A+C) = A + BC$$

$$\begin{aligned}
 &(A+B)(A+\bar{B})(\bar{A}+B)(\bar{A}+\bar{B}) \\
 &(A+B\bar{B})(\bar{A}+B\bar{B}) \quad \because B\bar{B}=0 \\
 &A.\bar{A} = 0 \quad \because A.\bar{A}=0
 \end{aligned}$$

$$\begin{aligned}
 &(x+y+z)(x+\bar{y}+\bar{z})(x+y+\bar{z}) \\
 &(x+y+z)(x+y+\bar{z})(x+\bar{y}+\bar{z}) \\
 &(x+y+z.\bar{z})(x+\bar{y}+\bar{z}) \quad \because z.\bar{z}=0 \\
 &(x+y)(x+\bar{y}+\bar{z}) \\
 &x+y(\bar{y}+\bar{z}) \\
 &x+y\bar{y}+y\bar{z} \quad \because y\bar{y}=0 \\
 &x+y\bar{z}
 \end{aligned}$$

⇒ Consensus Theorem

$$AB + \bar{A}C + BC = AB + \bar{A}C$$

$$(A+B)(\bar{A}+C)(B+C)$$

$$= (A+B)(\bar{A}+C)$$

$$AB + \bar{A}C \quad \text{R.F.}$$

Law of Consensus Theorem

$$AB + \bar{A}C + BC = AB + \bar{A}C$$

$$(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$$

$$(\bar{A}+\bar{B})(B+\bar{C})(\bar{A}+\bar{C})$$

$$= (\bar{A}+\bar{B})(B+\bar{C})$$

$$AB + \bar{A}\bar{B}CD$$

$$= (AB + \bar{A}\bar{B})(AB + CD)$$

$$= AB + CD$$

$$\because A + \bar{A} = 1$$

$$\because AB + \bar{A}\bar{B} = 1$$

$\Rightarrow$  Demorgan's Theorem

$$\overline{A+B} = \bar{A}\bar{B}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$(A+B)(A+B+C) + \bar{A}\bar{B}$$

$$(A+B+0)(A+B+C) + \bar{A}\bar{B}$$

$$(A+B+0 \cdot C) + \bar{A}\bar{B}$$

$$(A+B) + \bar{A}\bar{B}$$

~~$$A\bar{A}\bar{B} + \bar{A}\bar{B}B$$~~

~~$$= \bar{A}\bar{B}$$~~

$$A+B + \bar{A}\bar{B}$$

$$A+B(1+\bar{A}) = A+B$$

$$\because 0 \cdot C = 0$$

~~$$\because A \cdot \bar{A} = 0$$~~
~~$$B \cdot \bar{B} = 0$$~~

$$\because 1 + \bar{A} = 1$$

$$A + \bar{A}B + A\bar{B} = A + B$$

LHS  $A(1 + \bar{B}) + \bar{A}B$

$$\because 1 + \bar{B} = 1$$

$$A + \bar{A}B$$

$$(A + \bar{A})(A + B)$$

$$\because A + \bar{A} = 1$$

$$A + B = \underline{\underline{RHS}}$$

$$\Rightarrow A + \bar{A}B = A + B$$

Absorption Theorem

$$\bar{C} + CB = \bar{C} + B$$

$$[xy' + xyz + x(y + xy')]']$$

$$[xy' + xyz + xy + xy']'$$

$$\because x \cdot x = x$$

$$[xy' + xyz + xy]'$$

$$[xy' + xy(z + 1)]'$$

$$\because xy + xy = xy$$

$$[xy' + xy]'$$

$$\because z + 1 = 1$$

$$[x(y' + y)]' = x'$$

$$\because y' + y = 1$$



Minimise the exp and reduce the exp using logic gates

$$ABC + ABC\bar{C} + A\bar{B}\bar{C}$$

$$AB(C + \bar{C}) + A\bar{B}\bar{C}$$

$$AB + A\bar{B}\bar{C}$$

$$A(B + \bar{B}\bar{C})$$


$$A(B + \bar{C})$$

$$AB + A\bar{C}$$

$$\because C + \bar{C} = 1$$

$$\because B + \bar{B}\bar{C} = B + \bar{C}$$

[Absorption Th.]

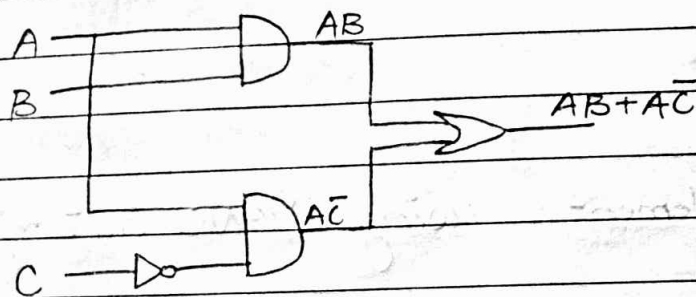

$$A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}\bar{C} + AB$$

$$A\bar{B}(C + \bar{C}) + AB(\bar{C} + 1)$$

$$A\bar{B} + AB$$

$$A(\bar{B} + B)$$

$$= A$$


$$C + \bar{C} = 1$$

$$\bar{C} + 1 = 1$$


$$\bar{B} + B = 1$$

$$A \text{ ——— } A$$


$AB + \overline{AB} + AC$

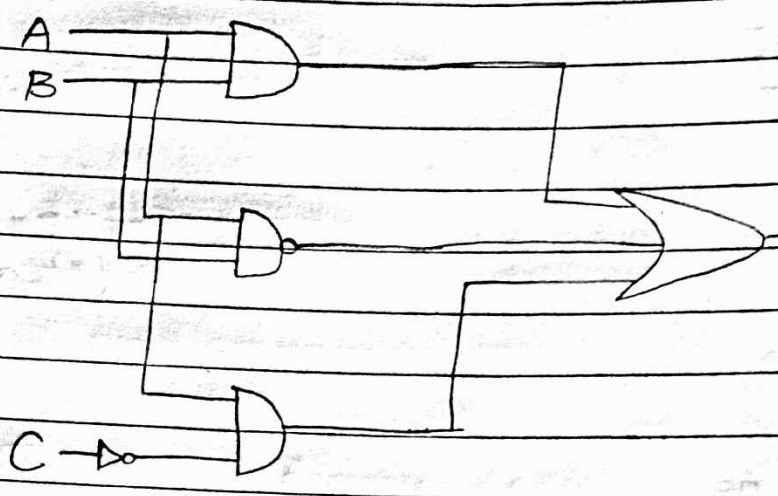

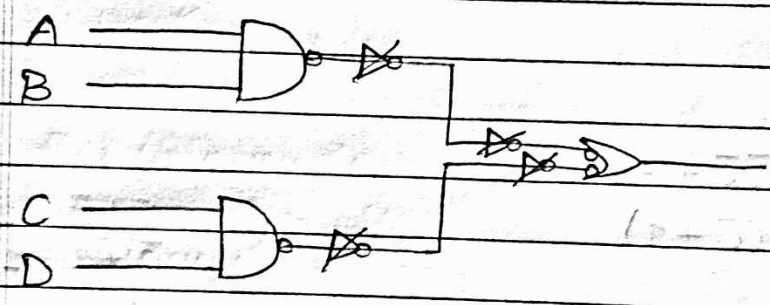
$AB + CD$  Implement using NAND Gate only




Final implementation: 7

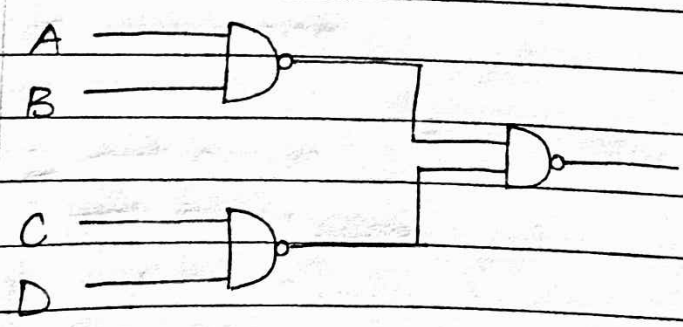

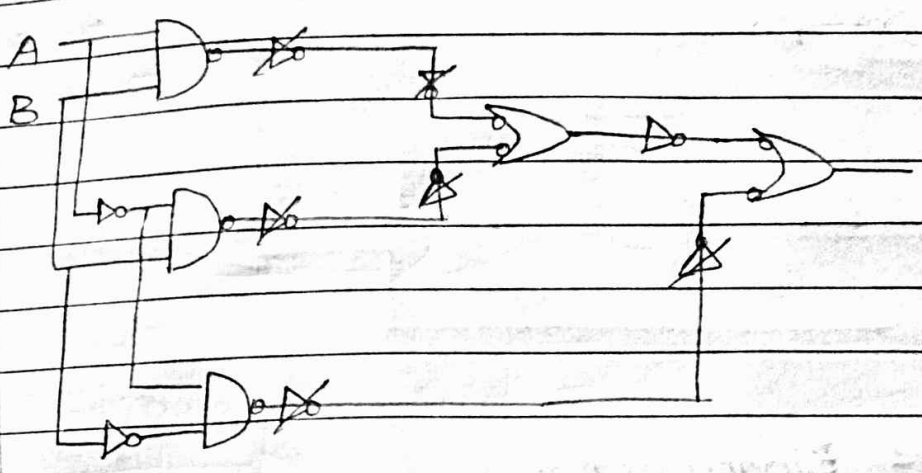
$AB + \bar{A}B + \bar{A}\bar{B}$  Implement only using NAND Gate




Final implementation

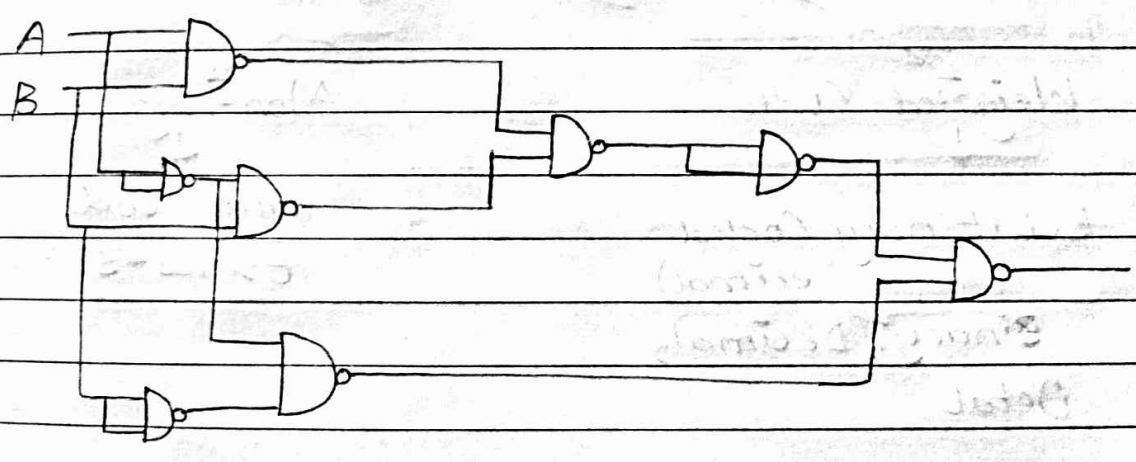

Using NOR Gate

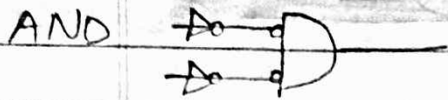

### Types of Binary Codes

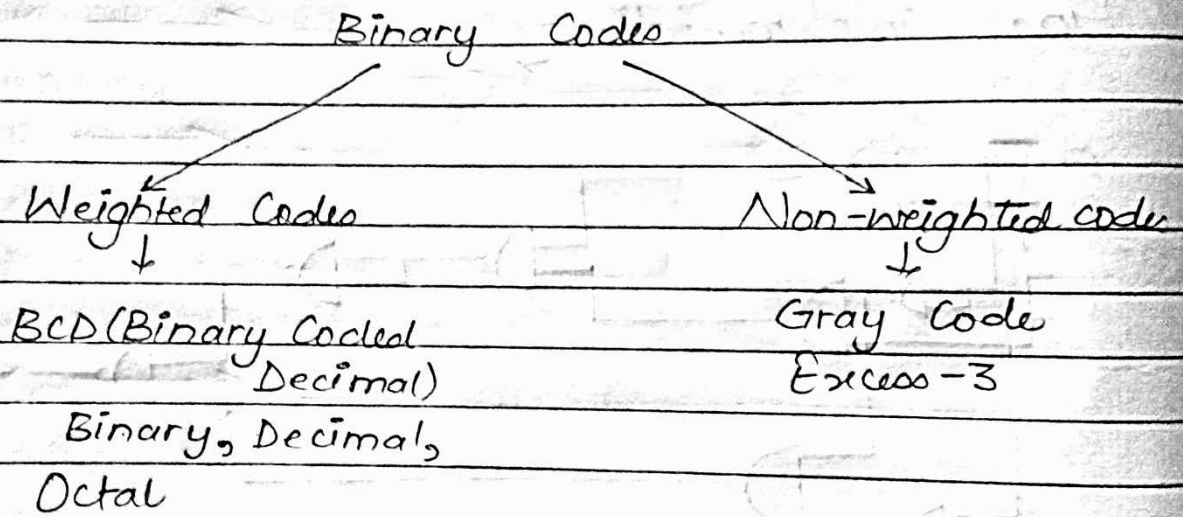

Example :-

BCD codes

- 0 → 0000
- 1 → 0001
- 2 → 0010
- 3 → 0011
- 4 → 0100
- 5 → 0101

Excess-3 (BCD + 0011)

- 0 → 0011
- 1 → 0100
- 2 → 0101
- 3 → 0110
- 4 → 0111
- 5 → 1000



Conversion :-

Binary to Gray

$11101 \rightarrow 10011$

[use XOR]

$1011001 \rightarrow 1110101$

Gray to Binary


1110101

↓ ↓ ↓ ↓ ↓


1011001

$1110101 \rightarrow 1011001$

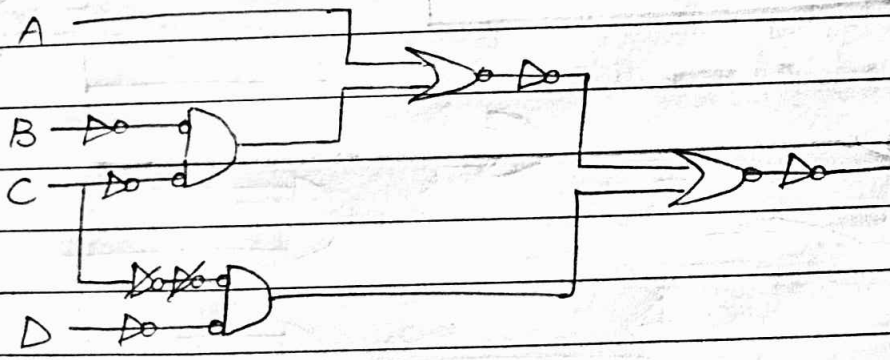
$A + BC + \bar{C}D$  Implement only using NOR Gate




Final implementation :-

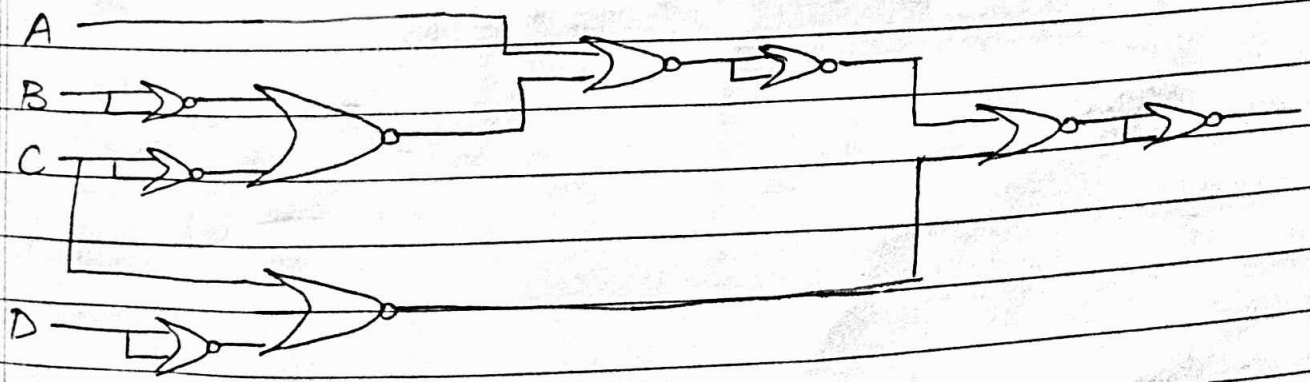

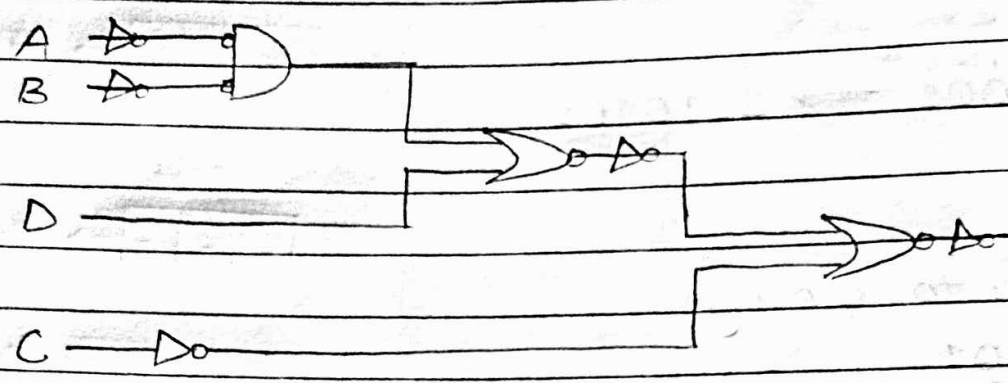$AB + D + \bar{C}$  Implement only using NOR



Final implementation







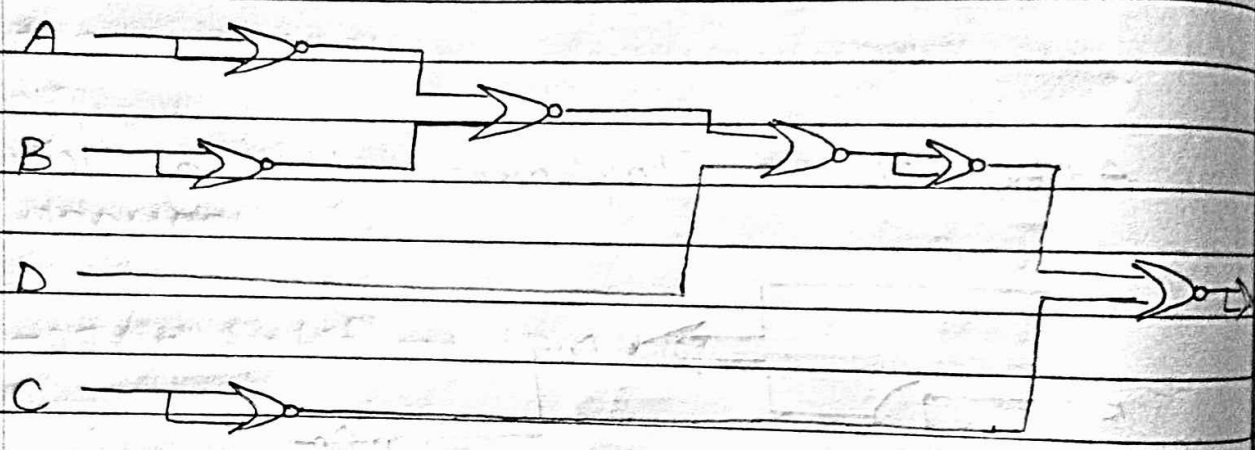


⇒ NAND and NOR are called universal gates because all the other gates can be made using these two gates

# Realisation of basic gates using universal gates

Using NAND

Using NOR

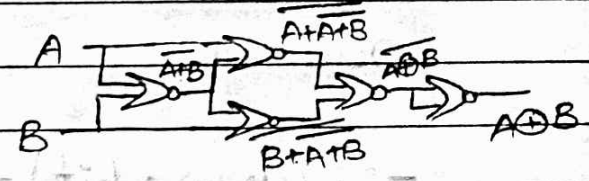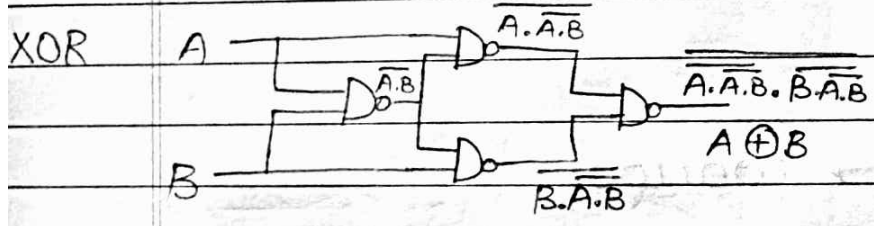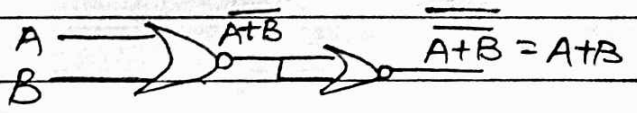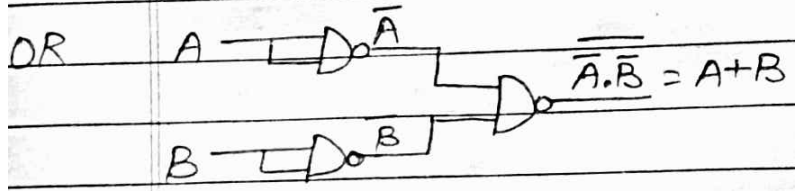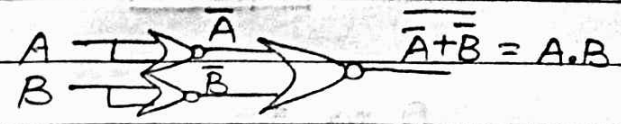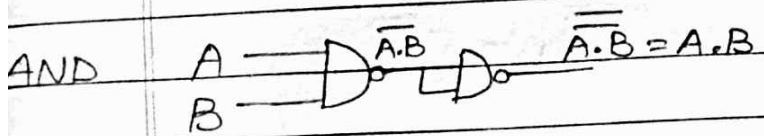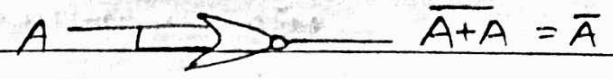

$$\overline{\overline{A \cdot \bar{B}} \cdot \overline{B \cdot \bar{A}}}$$



$$\overline{A \cdot \bar{B} + B \cdot \bar{A}}$$

$$\overline{\overline{A \oplus B}} = A \oplus B$$

$$A \cdot \bar{B} + B \cdot \bar{A} = A(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B})$$

~~$A \cdot \bar{A} + A \cdot \bar{B} + B \cdot \bar{A} + B \cdot \bar{B}$~~
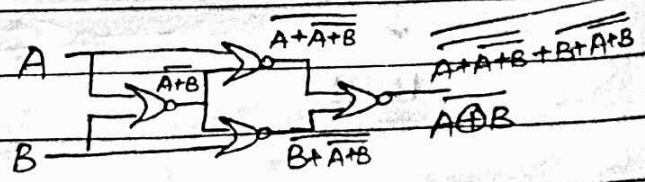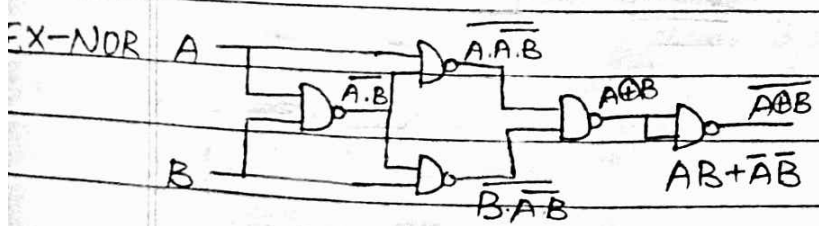
$$= A \cdot \bar{B} + \bar{A} \cdot B = A \oplus B$$





$$(A + \bar{A} + \bar{B})(\bar{B} + \bar{A} + B)$$

$$(A + \bar{A} \cdot \bar{B})(\bar{B} + \bar{A} \cdot B) = \bar{A} \cdot \bar{B}$$

$$= \overline{A \oplus B}$$



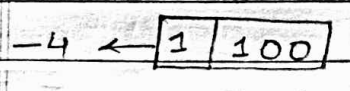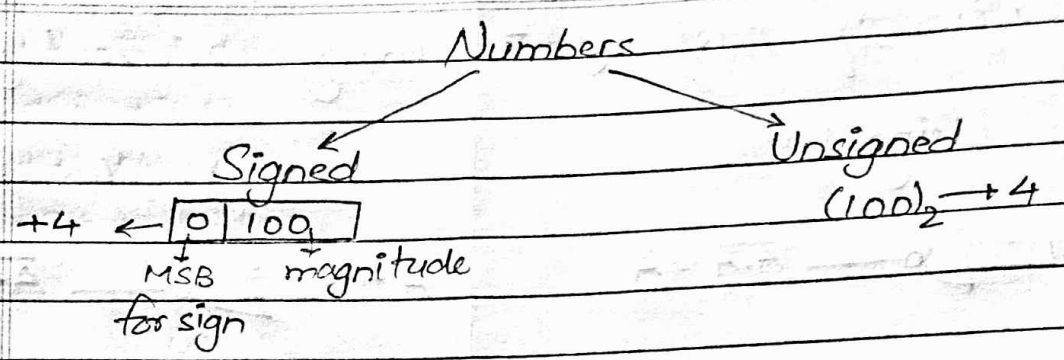

0 for +  
1 for -

+25 → 011001  
↓  
in 8 bit  
↓  
00011001

-25 (in 8-bit) → 10011001

1's complement  
-5 → 1101  
↓  
1's complement  
↓  
find the complement of +5 → 0101  
↓  
1010

Note: We always take 1's and 2's complement of a negative number.



Find 1's complement of

$$1010 \rightarrow 0101$$

$$001010 \rightarrow 110101$$

Find 2's complement of

~~1010~~

$$\begin{array}{r} 0101 \rightarrow 1010 \\ +1 \\ \hline 1011 \end{array}$$

Range of 1's complement

$$-(2^{n-1}-1) \text{ to } (2^{n-1}-1)$$

$n \rightarrow$  no. of bits

Find 1's complement of  $\pm 7$

$$-5$$

$$-7$$

$$+5 = 0101$$

$$+7 = 0111$$

$$-5 = 1010$$

$$-7 = 1000$$

Solve using 1's complement

Case 1:  $+5 - 4 = +1$

Range  $\rightarrow -7$  to  $+7$   
 $n = 4$

When  $+5 = 0101$

carry is generated,  $+4 = 0100$

add it to  $-4 = 1001$

LSB

$$\begin{array}{r} 0101 \\ +1011 \\ \hline 10000 \\ +1 \\ \hline 0001 \end{array}$$

[Add the carry to LSB]

$+7 - 3 = +4$

Range  $\rightarrow -7$  to  $+7$   
 $n = 4$

$+7 = 0111$

$+3 = 0011$

$-3 = 1100$

$$\begin{array}{r} 0111 \\ + 1100 \\ \hline 0011 \\ + 1 \\ \hline 0100 \rightarrow +4 \end{array}$$

$24 - 13 = +11$

Range  $\rightarrow -31$  to  $+31$   
 $n = 6$

$+24 = 011000$

$+13 = 001101$

$-13 = 110010$

$$\begin{array}{r} 011000 \\ + 110010 \\ \hline 001010 \\ + 1 \\ \hline 001011 \rightarrow +11 \text{ Ans} \end{array}$$

Case 2:  $-5 + 4 = -1$

Range  $\rightarrow -7$  to  $+7$   
 $n = 4$

When no carry is generated

$+5 = 0101$

$-5 = 1010$

$+4 = 0100$

and you have 1 on MSB, take

1's complement of the

$$\begin{array}{r} 1010 \\ + 0100 \\ \hline 1110 \\ \downarrow \end{array}$$

answer and

keep the

$-001 \rightarrow -1$

sign same.

$$-9 + 5 = -4$$

$$+9 = 01001$$

$$-9 = 10110$$

$$+5 = 00101$$

Range = -15 to 15  
n = 5

$$\begin{array}{r} 10110 \\ + 00101 \\ \hline 11011 \\ \downarrow \end{array}$$

10100 → -4 Ans

$$-44 + 12 = -32$$

$$+44 = 0101100$$

$$-44 = 1010011$$

$$+12 = 0001100$$

Range = -63 to 63  
n = 7

$$\begin{array}{r} 1010011 \\ + 0001100 \\ \hline 1011111 \\ \downarrow \end{array}$$

1100000 → -32 Ans

$-128 + 65 = -63$

$n=9$

$+128 = 010000000$

$-128 = 101111111$

$+65 = 001000001$

$$\begin{array}{r}
 \phantom{+} 1\ 1\ 1\ 1\ 1\ 1\ 1\ 1\ 1 \\
 1\ 0\ 1\ 1\ 1\ 1\ 1\ 1\ 1 \\
 +\ 0\ 0\ 1\ 0\ 0\ 0\ 0\ 0\ 1 \\
 \hline
 1\ 1\ 1\ 0\ 0\ 0\ 0\ 0\ 0 \\
 \downarrow
 \end{array}$$

$100111111 \rightarrow -63$  Ans

Case 3:  $-5 - 2 = -7$

$n=4$

combination of case 1  $+5 = 0101$

and case 2  $-5 = 1010$

$+2 = 0010$

$-2 = 1101$

$$\begin{array}{r}
 1\ 0\ 1\ 0 \\
 +\ 1\ 0\ 0\ 1 \\
 \hline
 0\ 1\ 1\ 1 \\
 +\ 1
 \end{array}$$

$1\ 0\ 0\ 0$

$\downarrow$

$1111 \rightarrow -7$  Ans



n=5

Case 4:  $-5 - 4 = -9$   
 $+5 = 00101$   
 $-5 = 11010$   
 $+4 = 00100$   
 $-4 = 11011$

$$\begin{array}{r} 11010 \\ \oplus 11011 \\ \hline 10101 \\ +1 \\ \hline 10110 \\ \downarrow \end{array}$$

11001  $\rightarrow$  -9 Ans

2's compliment  
 Range =  $-(2^{n-1})$  to  $(2^{n-1}-1)$

Case 1:  $+5 - 3 = +2$   
 Discard the carry  
 whenever + is generated  
 $+5 = 0101$   
 $+3 = 0011$   
 $-3 = 1100$   
 $+1$   
1101

Range = -8 to 7  
 n=4

$$\begin{array}{r} 0101 \\ + 1101 \\ \hline 0010 \end{array} \rightarrow +2 \text{ Ans}$$

Case 2:  $+2 - 6 = -4$

$n=4$

Whenever there is 1 on MSB take 2's complement

$$\begin{array}{r}
 +2 = 0010 \\
 +6 = 0110 \\
 -6 = 1001 \\
 \quad +1 \\
 \hline
 1010
 \end{array}$$

keeping sign same

$$\begin{array}{r}
 0010 \\
 + 1000 \\
 \hline
 1010 \\
 \downarrow \\
 \cancel{XXXX} \\
 1011 \\
 \quad +1 \\
 \hline
 1100 \rightarrow -4 \text{ Ans}
 \end{array}$$

Case 3:  $-5 - 2 = -7$

$n=4$

combination of case 1 and 2

$$\begin{array}{r}
 +5 = 0101 \\
 -5 = 1011 \\
 +2 = 0010 \\
 -2 = 1110
 \end{array}$$

$$\begin{array}{r}
 \oplus 1011 \\
 + 1110 \\
 \hline
 1001 \\
 \downarrow \\
 1111 \rightarrow -7 \text{ Ans}
 \end{array}$$


$$\begin{array}{r}
 1101 \\
 \quad +1 \\
 \hline
 1110
 \end{array}$$

$$\begin{array}{r}
 \oplus 110 \\
 \quad +1 \\
 \hline
 111
 \end{array}$$

Case 4:  $-5 - 4 = -9$   
 $+5 = 00101$   
 $-5 = 11011$   
 $+4 = 00100$   
 $-4 = 11100$

n=5
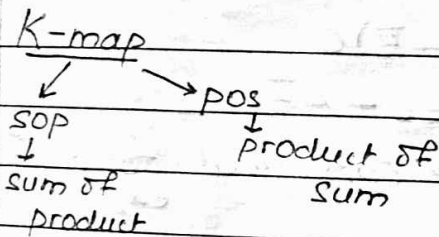
$$\begin{array}{r} 11011 \\ 0 \\ + 11100 \\ \hline 10111 \\ \downarrow \\ 11001 \rightarrow -9 \text{ Ans} \end{array}$$



SOP

Sum of Products

Minterms (m)

$\sum m$

$0 \rightarrow \bar{A}$

$1 \rightarrow A$

$ABC + \bar{A}\bar{B}C + \bar{A}B\bar{C} \rightarrow \text{SOP}$

POS

Product of Sum

Maxterms (M)

$\prod M$

$0 \rightarrow A$

$1 \rightarrow \bar{A}$

$(A+B+\bar{C})(A+B+C) \rightarrow \text{POS}$

0 →  $\bar{A}$   
1 → A

0 → A  
1 →  $\bar{A}$

$x y z$	Minterms (SOP)	Maxterms (POS)
0 0 0	$\bar{x}\bar{y}\bar{z}$ $m_0$	$x+y+z$ $M_0$
0 0 1	$\bar{x}\bar{y}z$ $m_1$	$x+y+\bar{z}$ $M_1$
0 1 0	$\bar{x}y\bar{z}$ $m_2$	$x+\bar{y}+z$ $M_2$
0 1 1	$\bar{x}yz$ $m_3$	$x+\bar{y}+\bar{z}$ $M_3$
1 0 0	$x\bar{y}\bar{z}$ $m_4$	$\bar{x}+y+z$ $M_4$
1 0 1	$x\bar{y}z$ $m_5$	$\bar{x}+y+\bar{z}$ $M_5$
1 1 0	$xy\bar{z}$ $m_6$	$\bar{x}+\bar{y}+z$ $M_6$
1 1 1	$xyz$ $m_7$	$\bar{x}+\bar{y}+\bar{z}$ $M_7$

Canonical form (Standard form)

$$BC + A\bar{B} + AC$$

$$(A + \bar{A})BC + A\bar{B}(C + \bar{C}) + A(B + \bar{B})C$$

$$ABC + \bar{A}BC + A\bar{B}C + A\bar{B}\bar{C} + ABC + A\bar{B}C$$

$$ABC + \bar{A}BC + A\bar{B}C + A\bar{B}\bar{C} \rightarrow \text{canonical form of exp}$$

$111$     $011$     $101$     $100$   
 $m_7$     $m_3$     $m_5$     $m_4$

$\sum m(3, 4, 5, 7) \rightarrow$  standard form

$$A\bar{B} + B + BC$$

$$A\bar{B}(C + \bar{C}) + (A + \bar{A})B(C + \bar{C}) + (A + \bar{A})BC$$

$$A\bar{B}C + A\bar{B}\bar{C} + ABC + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}B\bar{C} + ABC + \bar{A}BC$$

$$A\bar{B}C + A\bar{B}\bar{C} + ABC + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}B\bar{C}$$

$101$     $100$     $111$     $110$     $011$     $010$   
 $m_5$     $m_4$     $m_7$     $m_6$     $m_3$     $m_2$

$\sum m(2, 3, 4, 5, 6, 7)$



$$ABC\bar{D} + A\bar{B}D + A\bar{B}\bar{D}$$

$$ABC(D+\bar{D}) + A\bar{B}(C+\bar{C})D + A\bar{B}(C+\bar{C})\bar{D}$$

$$ABC\bar{D} + ABCD + A\bar{B}C\bar{D} + A\bar{B}CD + A\bar{B}C\bar{D} + A\bar{B}C\bar{D}$$

$$\begin{array}{cccccc} 1101 & 1100 & 1011 & 1001 & 1010 & 1000 \\ m_{13} & m_{12} & m_{11} & m_9 & m_{10} & m_8 \end{array}$$

$$\sum m(8, 9, 10, 11, 12, 13)$$

$$(A+B)(A+\bar{C})$$

$$(A+B+C\bar{C})(A+B\bar{B}+\bar{C})$$

$$(A+B+C)(A+B+\bar{C})(A+B+\bar{C})(A+\bar{B}+\bar{C})$$

$$(A+B+C)(A+B+\bar{C})(A+\bar{B}+\bar{C})$$

$$000 \quad 001 \quad 011$$

$$M_0 \quad M_1 \quad M_3$$

$$\sum M(0, 1, 3)$$

$$(A+B)(\bar{B}+C)(\bar{A}+\bar{C})$$

$$(A+B+C\bar{C})(A\bar{A}+\bar{B}+C)(\bar{A}+B\bar{B}+\bar{C})$$

$$(A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})(\bar{A}+\bar{B}+\bar{C})$$

$$000 \quad 001 \quad 010 \quad 110 \quad 101 \quad 111$$

$$M_0 \quad M_1 \quad M_2 \quad M_6 \quad M_5 \quad M_7$$

$$\sum M(0, 1, 2, 5, 6, 7)$$

$ABC + CD + A\bar{B}D$  → find maxterms

$ABC(D + \bar{D}) + (A + \bar{A})(B + \bar{B})CD + A\bar{B}(C + \bar{C})D$

$ABCD + ABC\bar{D} + A\bar{B}CD + A\bar{B}\bar{C}D + \bar{A}BCD + \bar{A}\bar{B}CD + \bar{A}BC\bar{D} + \bar{A}\bar{B}\bar{C}D$

~~XXXX~~ ~~XXXX~~ ~~XXXX~~ ~~A~~ ~~1111~~ ~~1111~~ ~~1111~~ ~~1111~~ ~~1111~~ ~~1111~~

$ABCD + ABC\bar{D} + \bar{A}BCD + \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}D$

1111 1110 1011 0111 0011 0001

$m_{15}$   $m_{14}$   $m_{11}$   $m_7$   $m_3$   $m_9$

$\Sigma M(0, 2, 4, 5, 6, 8, 10, 12, 13)$

K-map

2-variable

$2^2 = 4$



4 cells

3-variable

$2^3 = 8$



8 cells

4-variable

$2^4 = 16$



16 cells

2-variable K-map

	B	0	1
A	0	00 <sup>0</sup>	01 <sup>1</sup>
	1	10 <sup>2</sup>	11 <sup>3</sup>

SOP

	B	0	1
$\bar{A}$	0	0	1
A	1	2	3

POC

	B	0	1
A	0	0	1
$\bar{A}$	1	2	3

### 3-variable K-Map

	BC	00	01	11	10
A		0	1	3	2
0		000	001	011	010
1		100	101	111	110

00 → 1  
01 → 1  
11 → 1  
10 → 2

↓  
Gray code pattern

↓  
Change of one bit b/w two consecutive numbers

SOP ↓

	BC	$\bar{B}\bar{C}$	$\bar{B}C$	$BC$	$B\bar{C}$
A		00	01	11	10
$\bar{A}$ 0		0	1	3	2
A 1		4	5	7	6

POS ↓

	BC	$B+C$	$B+\bar{C}$	$\bar{B}+C$	$\bar{B}+\bar{C}$
A		00	01	11	10
A 0		0	1	3	2
$\bar{A}$ 1		4	5	7	6

### 4-variable K-map

	CD	00	01	11	10
AB		0	1	3	2
00		0000	0001	0011	0010
01		0100	0101	0111	0110
11		1100	1101	1111	1110
10		1000	1001	1011	1010



4-variable

SOP  $\downarrow$ 

AB \ CD	$\bar{C}\bar{D}$ 00	$\bar{C}D$ 01	$CD$ 11	$C\bar{D}$ 10
$\bar{A}\bar{B}$ 00	0	1	3	2
$\bar{A}B$ 01	4	5	7	6
$AB$ 11	12	13	15	14
$A\bar{B}$ 10	8	9	11	10

POS  $\downarrow$ 

AB \ CD	$C+D$ 00	$C+\bar{D}$ 01	$\bar{C}+D$ 11	$\bar{C}+\bar{D}$ 10
$A+B$ 00	0	1	3	2
$A+\bar{B}$ 01	4	5	7	6
$\bar{A}+\bar{B}$ 11	12	13	15	14
$\bar{A}+B$ 10	8	9	11	10

Note: Minterms are denoted using 1 and maxterms using 0.

Note: Diagonal pairing can't be there in K-map



Reduce the boolean expression using K-map

$$\bar{A}B + A\bar{B} + \bar{A}\bar{B}$$

01 10 00  
m<sub>1</sub> m<sub>2</sub> m<sub>0</sub>

$$\sum m(1, 2, 0)$$

A \ B	0	1
0	1	1
1	1	0

$$Y = A + \bar{B}$$

~~$\sum m(1, 2, 3)$~~

A \ B	0	1
0	1	1
1	1	1

$$Y = A + \bar{B}$$

$$\sum m(1, 2, 3)$$

A \ B	0	1
0	0	1
1	1	1

$$Y = A + B$$



A \ B	1 <sup>0</sup>	1 <sup>1</sup>	Y = 1
	1 <sup>2</sup>	1 <sup>3</sup>	

A \ BC	1 <sup>0</sup>	1 <sup>1</sup>	1 <sup>3</sup>	1 <sup>2</sup>	Y = 1
	1 <sup>4</sup>	1 <sup>5</sup>	1 <sup>7</sup>	1 <sup>6</sup>	

Note: Priority in pairing is first given to octet, then to quad then to pair.

$$\bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}C + ABC$$

$$011 \quad 110 \quad 001 \quad 100 \quad 111$$

$$m_3 \quad m_6 \quad m_1 \quad m_4 \quad m_7$$

$$\Sigma m(1, 3, 4, 6, 7)$$

A \ BC	00	01	11	10
0	0	1 <sup>1</sup>	1 <sup>3</sup>	2
1	1 <sup>4</sup>	5	1 <sup>7</sup>	1 <sup>6</sup>

$$Y = \bar{A}C + BC + A\bar{C}$$

Redundant pair

In any octet, quad or pair there should be minimum one minterm (1) or maxterm (0) that is not involved in any other pairing.


~~$$\Sigma m(1, 2, 3, 6, 7, 8)$$~~

~~| AB \ CD | 00             | 01             | 11             | 10             |
|---------|----------------|----------------|----------------|----------------|
| 00      | 0              | 1 <sup>1</sup> | 1 <sup>3</sup> | 1 <sup>2</sup> |
| 01      | 4              | 5              | 1 <sup>7</sup> | 1 <sup>6</sup> |
| 11      | 12             | 13             | 15             | 14             |
| 10      | 1 <sup>8</sup> | 9              | 11             | 10             |~~

$\Sigma m(1, 2, 3, 6, 7)$

	BC	00	01	11	10
A	0	0	1 <sup>1</sup>	1 <sup>3</sup>	1 <sup>2</sup>
1	4	5	1 <sup>7</sup>	1 <sup>6</sup>	

$Y = B + \bar{A}C$

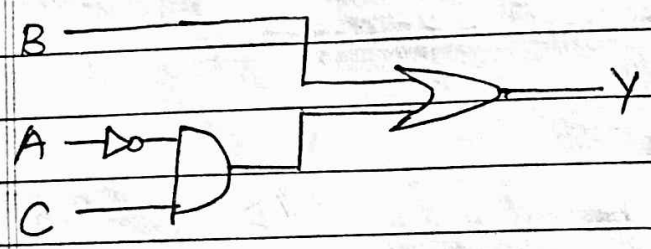


$\bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}$   
 101 011 111 ~~110~~ 001 100  
 $m_5 \quad m_3 \quad m_7 \quad m_6 \quad m_1 \quad m_4$

$\Sigma m(1, 3, 4, 5, 6, 7)$

	BC	00	01	11	10
A	0	0	1 <sup>1</sup>	1 <sup>3</sup>	2
1	4	1 <sup>4</sup>	1 <sup>5</sup>	1	1 <sup>6</sup>

$Y = A + C$

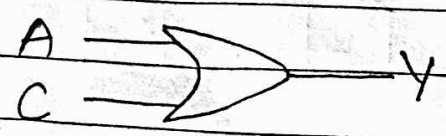



$$(A+B+\bar{C})(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+\bar{C})(A+B+C)(\bar{A}+\bar{B}+C)(A+\bar{B}+C)$$

0 0 1 0 1 1 1 1 1 0 0 0 1 1 0 0 1 0


$M_1$      $M_3$      $M_7$      $M_0$      $M_6$      $M_2$

$$\Sigma M(1, 1, 2, 3, 6, 7)$$

A \ BC	00	01	11	10
0	0 <sup>0</sup>	0 <sup>1</sup>	0 <sup>3</sup>	0 <sup>2</sup>
1	4	5	0 <sup>7</sup>	0 <sup>6</sup>

$$Y = A\bar{B}$$

~~Y = A\bar{B}~~

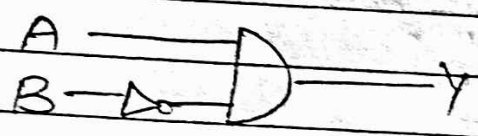

$$\Sigma m(1, 2, 3, 5, 6, 7, 9, 10, 12, 13, 15)$$

AB \ CD	00	01	11	10
00	0	1 <sup>1</sup>	1 <sup>3</sup>	1 <sup>2</sup>
01	4	1 <sup>5</sup>	1 <sup>7</sup>	1 <sup>6</sup>
11	1 <sup>12</sup>	1 <sup>13</sup>	1 <sup>15</sup>	1 <sup>14</sup>
10	8	1 <sup>9</sup>	1 <sup>11</sup>	1 <sup>10</sup>

$$Y = CD + \bar{A}C + \bar{A}D + \bar{B}D + \bar{B}C + ABC\bar{D}$$



$\Sigma M(1, 3, 5, 6, 9, 10)$ 

Reduce exp using K-map and find the ans in SOP

 $\Sigma m(0, 2, 4, 7, 8, 11, 12, 13, 14, 15)$ 

AB \ CD	00	01	11	10
00	1 <sup>0</sup>			1 <sup>2</sup>
01	1 <sup>4</sup>	5	1 <sup>7</sup>	6
11	1 <sup>12</sup>	1 <sup>13</sup>	1 <sup>15</sup>	1 <sup>14</sup>
10	1 <sup>8</sup>	9	1 <sup>11</sup>	10

$$Y = \bar{C}\bar{D} + AB + ACD + BCD + \bar{A}\bar{B}\bar{D}$$

$\Sigma m(0, 1, 2, 3, 5, 6, 9)$  Reduce the exp using K-map and find the ans in POS

 $\Sigma M(4, 7, 8, 10, 11, 12, 13, 14, 15)$ 

AB \ CD	00	01	11	10
00	0	1		2
01	0 <sup>4</sup>	5	0 <sup>7</sup>	6
11	0 <sup>12</sup>	0 <sup>13</sup>	0 <sup>15</sup>	0 <sup>14</sup>
10	0 <sup>8</sup>	9	0 <sup>11</sup>	0 <sup>10</sup>

$$Y = (\bar{A} + \bar{B})(\bar{A} + \bar{C})(\bar{B} + \bar{C} + \bar{D})(\bar{A} + D)(\bar{B} + C + D)$$

$\sum m(0, 1, 2, 3, 5, 9, 10, 12, 14, 15)$

AB \ CD	00	01	11	10
00	1 <sup>0</sup>	1 <sup>1</sup>	1 <sup>3</sup>	1 <sup>2</sup>
01	4	1 <sup>5</sup>	7	6
11	1 <sup>2</sup>	13	1 <sup>15</sup>	1 <sup>14</sup>
10	8	1 <sup>9</sup>	11	1 <sup>10</sup>

$Y = \bar{A}\bar{B} + \bar{A}\bar{C}D + \bar{B}\bar{C}D + AB\bar{D} + ABC + ACD$

$\sum m(1, 3, 5, 7, 13, 15, 9, 11) + d(4, 6)$

↓  
don't care terms

AB \ CD	00	01	11	10
00	0	1 <sup>1</sup>	1 <sup>3</sup>	2
01	X <sup>4</sup>	1 <sup>5</sup>	1 <sup>7</sup>	X <sup>6</sup>
11	12	1 <sup>13</sup>	1 <sup>15</sup>	1 <sup>14</sup>
10	8	1 <sup>9</sup>	1 <sup>11</sup>	10

$Y = D + BC$

Note: No two or more than two don't care terms can pair <sup>among</sup> themselves.

$$\sum m(1, 3, 5, 6, 10, 11, 12, 13, 14) + d(7, 0)$$

AB \ CD	00	01	11	10
00	X <sup>0</sup>	1 <sup>1</sup>	1 <sup>3</sup>	2
01	4	1 <sup>5</sup>	X <sup>7</sup>	1 <sup>6</sup>
11	1 <sup>12</sup>	1 <sup>13</sup>	15	1 <sup>14</sup> → Reduntant pāi
10	8	9	1 <sup>11</sup>	1 <sup>10</sup>


$$Y = \bar{A}D + ABC\bar{C} + BCD\bar{D} + A\bar{B}C$$

# UNIT-2

## Digital Circuits

- Combinational
- Sequential

### Combinational

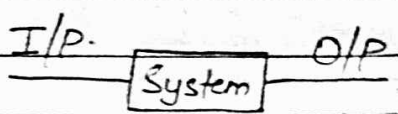

→ Here, output depends only on present input.

→ No memory element


→ No feedback

→ Time independent

→ Fast

→ Not complex

### Sequential

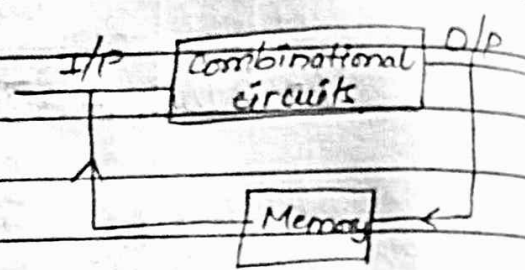

Output depends on the present input as well as the past outputs.

Feedback given through the memory element.

Time dependent

Slow


Complex



Note: Basic building block of logic gate  $\rightarrow$  Flip flop

Half adder [2-bit addition]

I. Block diagram

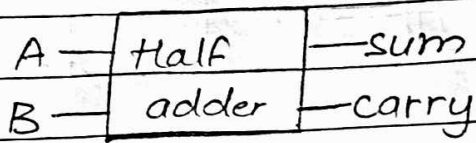

II Truth Table

A	B	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

III Expression for sum and carry

Exp for sum

A \ B	0	1
0	0	1
1	1	0


$$\text{sum} = \bar{A}B + A\bar{B} = A \oplus B$$

Exp for carry

A \ B	0	1
0	0	0
1	0	1


$$\text{carry} = AB$$
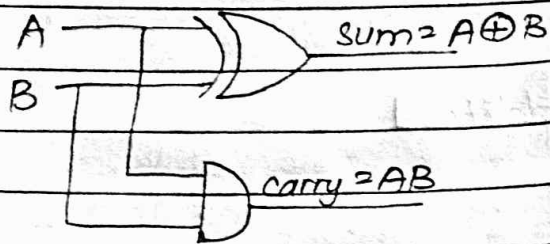
### IV Implementation of ~~imp~~ half adder



### Full Adder

#### I. Block diagram

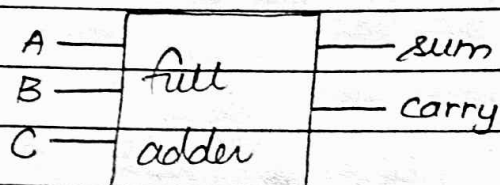

#### II Truth Table

A	B	C	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{sum} = \sum m(1, 2, 4, 7)$$

$$\text{carry} = \sum m(3, 5, 6, 7)$$

### III Exp for sum

A \ BC	00	01	11	10
0	0	1	3	1
1	4	5	7	6

$$\text{sum} = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC = \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC)$$

$$\bar{A}(B \oplus C) + A(\overline{B \oplus C})$$

Let  $B \oplus C = x$

$$\bar{A}x + A\bar{x} = A \oplus x$$

$$= A \oplus B \oplus C$$

### Exp for carry


A \ BC	00	01	11	10
0	0		1	
1	4	5	7	6

Carry =  $\bar{A}BC + AB\bar{C} + ABC$


$$\text{Carry} = AC + AB + BC$$

### IV Implementing using AOI


$$\text{sum} = A \oplus B \oplus C$$

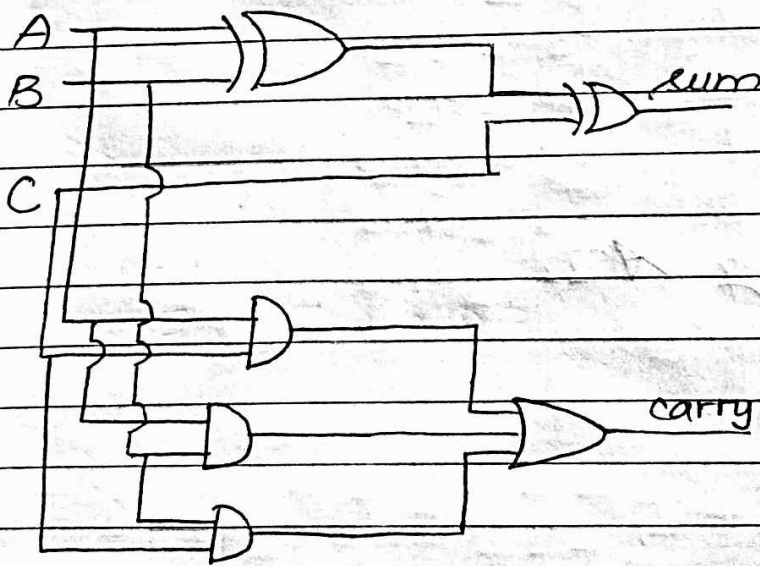

## Combinational Circuits

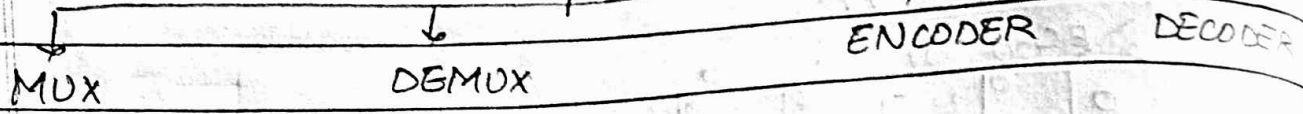

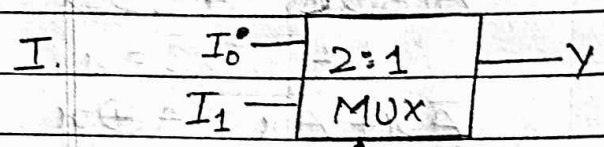Multiplexer → MUX → Many to One  
2:1 MUX



no. of select lines  
2:1 → outputs  
input

S → select line

↓  
decide which data will be routed as output


### II. Truth Table

I	S	Y
$I_0$	0	$I_0 \bar{S}$
$I_1$	1	$I_1 S$

### III. Expression


$$Y = I_0 \bar{S} + I_1 S$$

### IV. Implementing using AOT

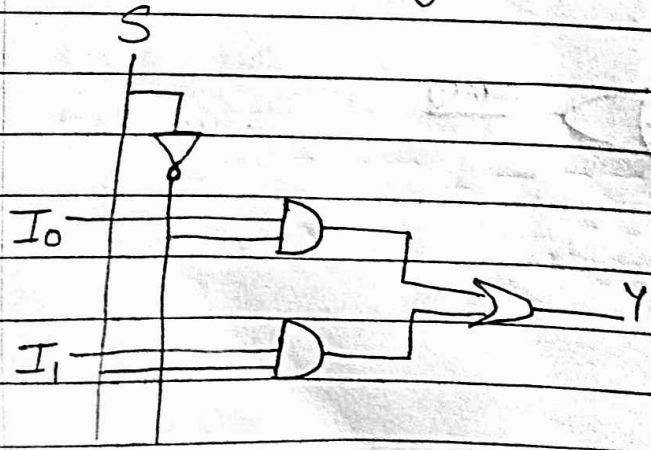



### 4:1 MUX

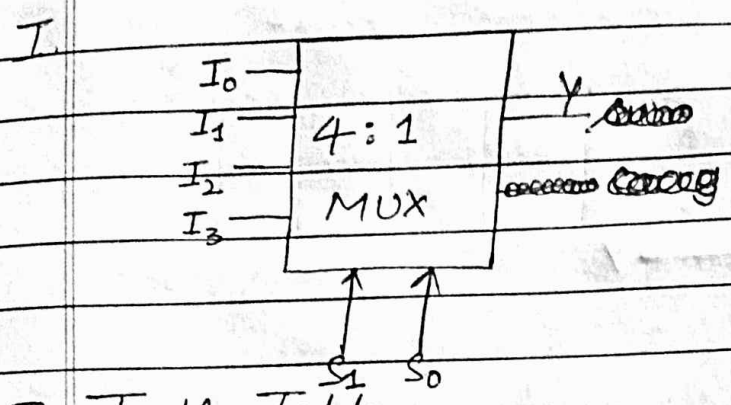


### II. Truth Table

I	S <sub>1</sub>	S <sub>0</sub>	Y
I <sub>0</sub>	0	0	$I_0 \bar{S}_1 \bar{S}_0$
I <sub>1</sub>	0	1	$I_1 \bar{S}_1 S_0$
I <sub>2</sub>	1	0	$I_2 S_1 \bar{S}_0$
I <sub>3</sub>	1	1	$I_3 S_1 S_0$


### III Expression

$$Y = I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0$$

### IV Implementing using AOI

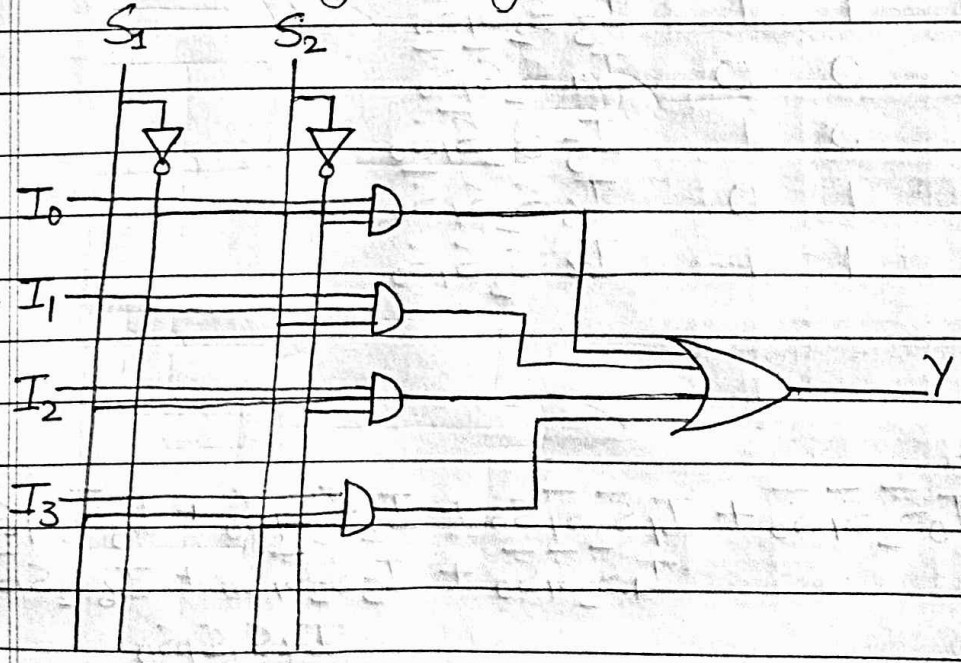

### 8:1 MUX

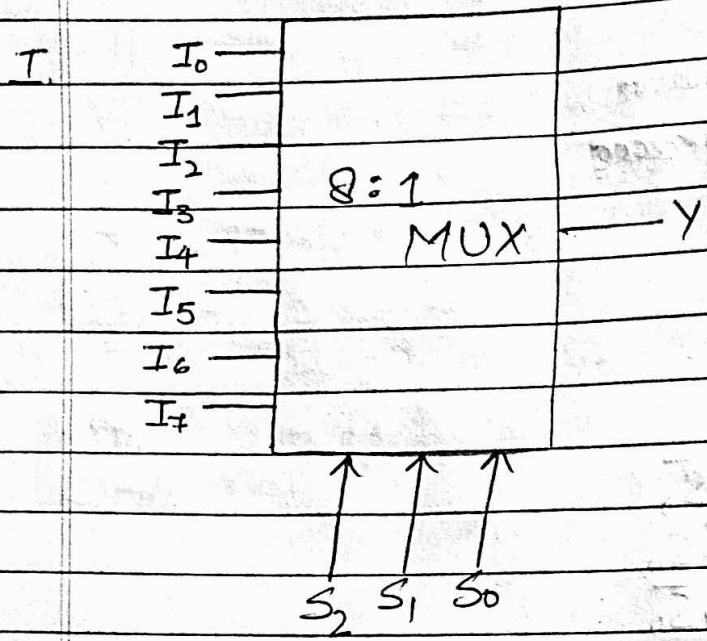


### II Truth Table

I	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y
I <sub>0</sub>	0	0	0	$I_0 \bar{S}_2 \bar{S}_1 \bar{S}_0$
I <sub>1</sub>	0	0	1	$I_1 \bar{S}_2 \bar{S}_1 S_0$
I <sub>2</sub>	0	1	0	$I_2 \bar{S}_2 S_1 \bar{S}_0$
I <sub>3</sub>	0	1	1	$I_3 \bar{S}_2 S_1 S_0$
I <sub>4</sub>	1	0	0	$I_4 S_2 \bar{S}_1 \bar{S}_0$
I <sub>5</sub>	1	0	1	$I_5 S_2 \bar{S}_1 S_0$
I <sub>6</sub>	1	1	0	$I_6 S_2 S_1 \bar{S}_0$
I <sub>7</sub>	1	1	1	$I_7 S_2 S_1 S_0$

### III Expression

$$Y = I_0 \bar{S}_2 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_2 \bar{S}_1 S_0 + I_2 \bar{S}_2 S_1 \bar{S}_0 + I_3 \bar{S}_2 S_1 S_0 + I_4 S_2 \bar{S}_1 \bar{S}_0 + I_5 S_2 \bar{S}_1 S_0 + I_6 S_2 S_1 \bar{S}_0 + I_7 S_2 S_1 S_0$$

### IV Implementing using AOI

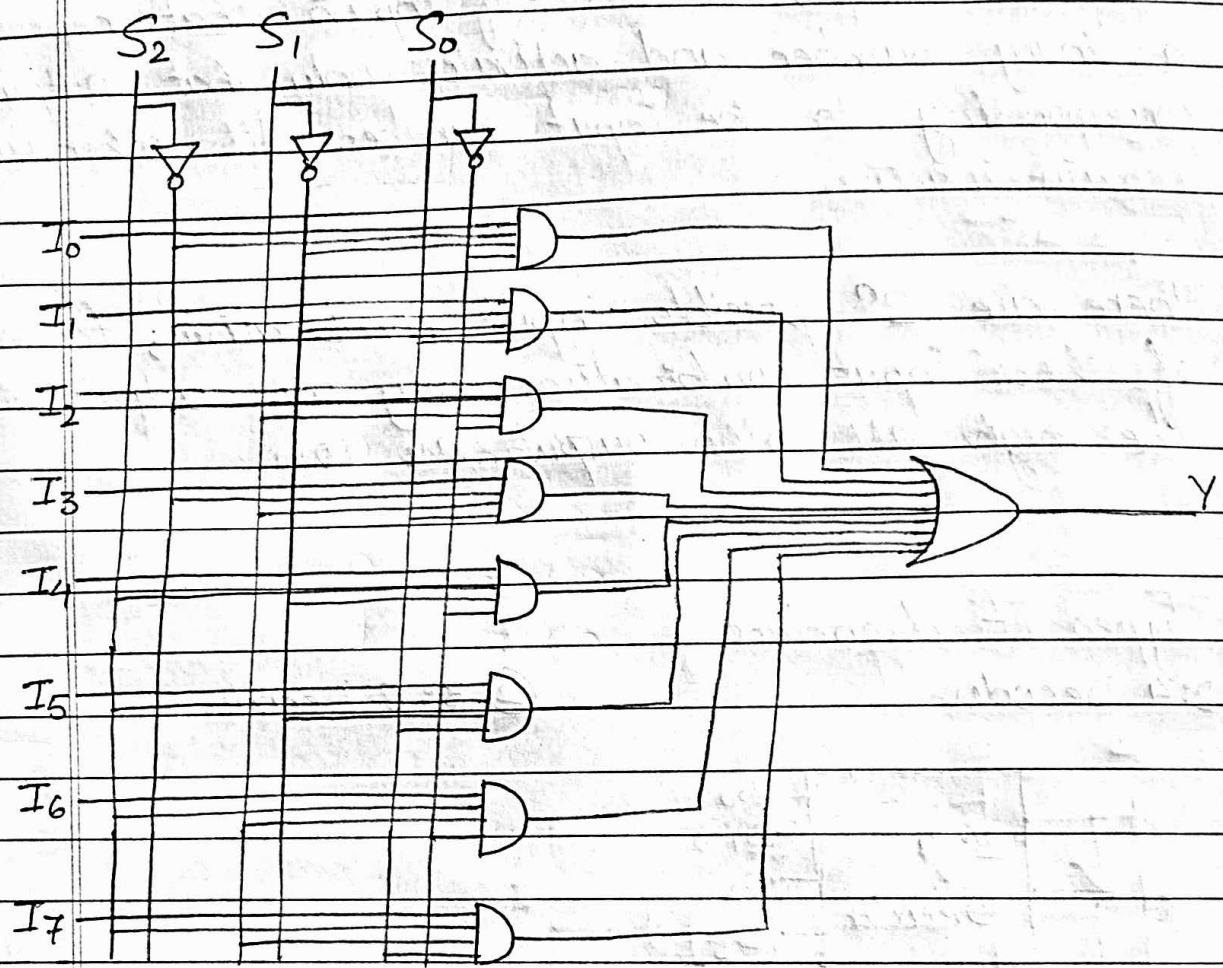



## Decoder

A decoder is a combinational circuit.


A decoder accepts a set of inputs that represent a binary number and activates only that output corresponding to the input number. All other outputs remain inactive.

There are  $2^n$  possible input combinations, for each of these input combinations only one output will be high all other outputs are low.

### Types of decoders

① 2:4 Decoder

② 3:8 Decoder

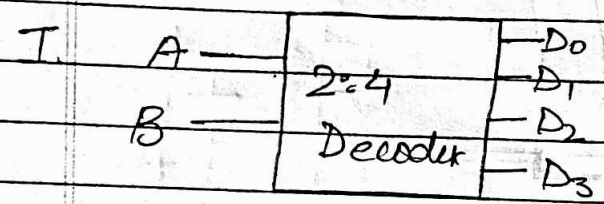

II	A	B	$D_0$	$D_1$	$D_2$	$D_3$
	0	0	1	0	0	0
	0	1	0	1	0	0
	1	0	0	0	1	0
	1	1	0	0	0	1

### III Expression

$$D_0 = \bar{A}\bar{B}$$

$$D_1 = \bar{A}B$$

$$D_2 = A\bar{B}$$

$$D_3 = AB$$





### III. Expression

$$D_0 = \bar{A}\bar{B}\bar{C}$$

$$D_1 = \bar{A}\bar{B}C$$

$$D_2 = \bar{A}B\bar{C}$$

$$D_3 = \bar{A}BC$$


$$D_4 = A\bar{B}\bar{C}$$

$$D_5 = A\bar{B}C$$

$$D_6 = ABC\bar{C}$$


$$D_7 = ABC$$

### IV. Implementing using AOT

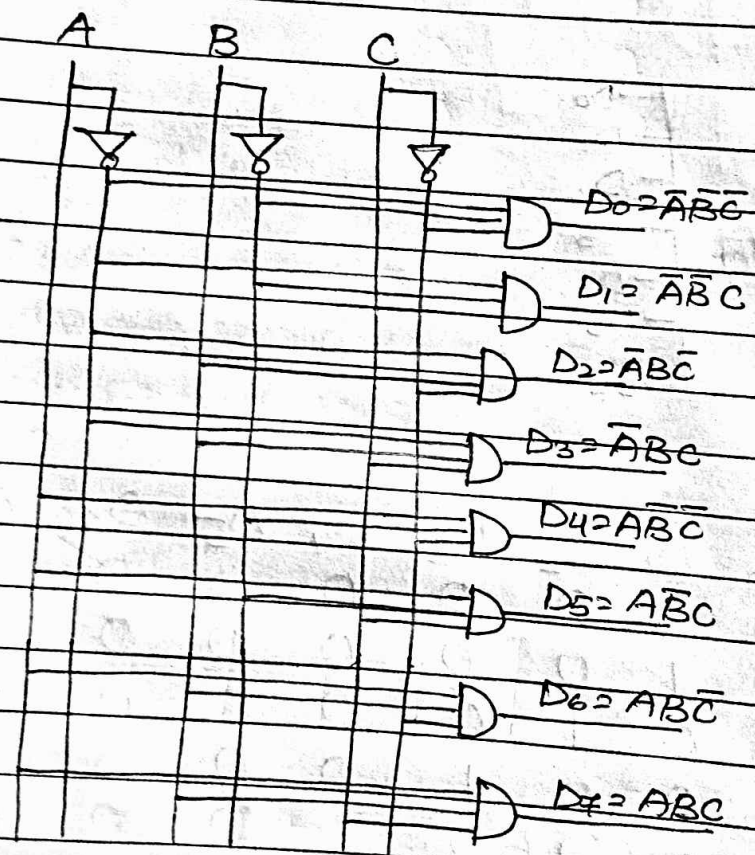

## Subtractor

## Half subtractor

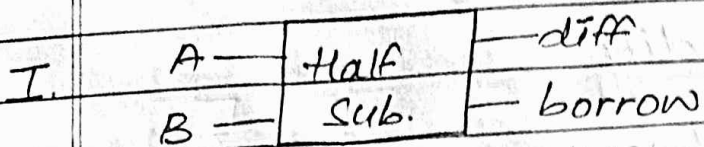

## II Truth Table

A	B	diff	borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

## III Expression

Exp for diff

A \ B	0	1
0	0 <sup>1</sup>	1 <sup>1</sup>
1	1 <sup>2</sup>	3


$$\text{diff} = \bar{A}B + A\bar{B} = A \oplus B$$

Exp for borrow

A \ B	0	1
0	0 <sup>1</sup>	1 <sup>1</sup>
1	2	3

$$\text{borrow} = \bar{A}B$$


## IV Implementing

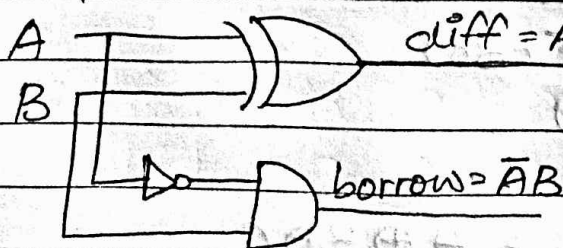



# Full Subtractor

## T. Block diagram

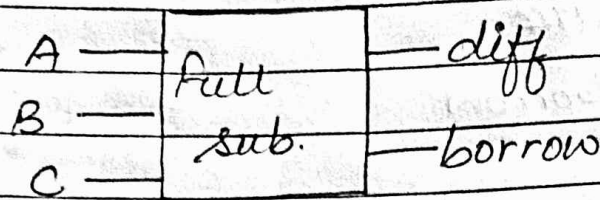

## II. Truth Table

A	B	C	diff	borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

## III. Expression

$$\text{diff} = \sum m(1, 2, 4, 7)$$

$$\text{carry} = \sum m(1, 2, 3, 7)$$

Exp for diff

A \ BC	00	01	11	10
0	0 <sup>0</sup>	1 <sup>1</sup>	3 <sup>3</sup>	1 <sup>2</sup>
1	1 <sup>4</sup>	5 <sup>5</sup>	1 <sup>7</sup>	6 <sup>6</sup>

$$\text{diff} = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC)$$

$$= \bar{A}(B \oplus C) + A(\overline{B \oplus C})$$

$$\text{let } B \oplus C = x$$


$$\bar{A}x + A\bar{x} = A \oplus x = A \oplus B \oplus C$$



Exp for borrow

A	BC	00	01	11	10
0		0	1 <sup>1</sup>	1 <sup>3</sup>	1 <sup>2</sup>
1		4	5	1 <sup>7</sup>	6

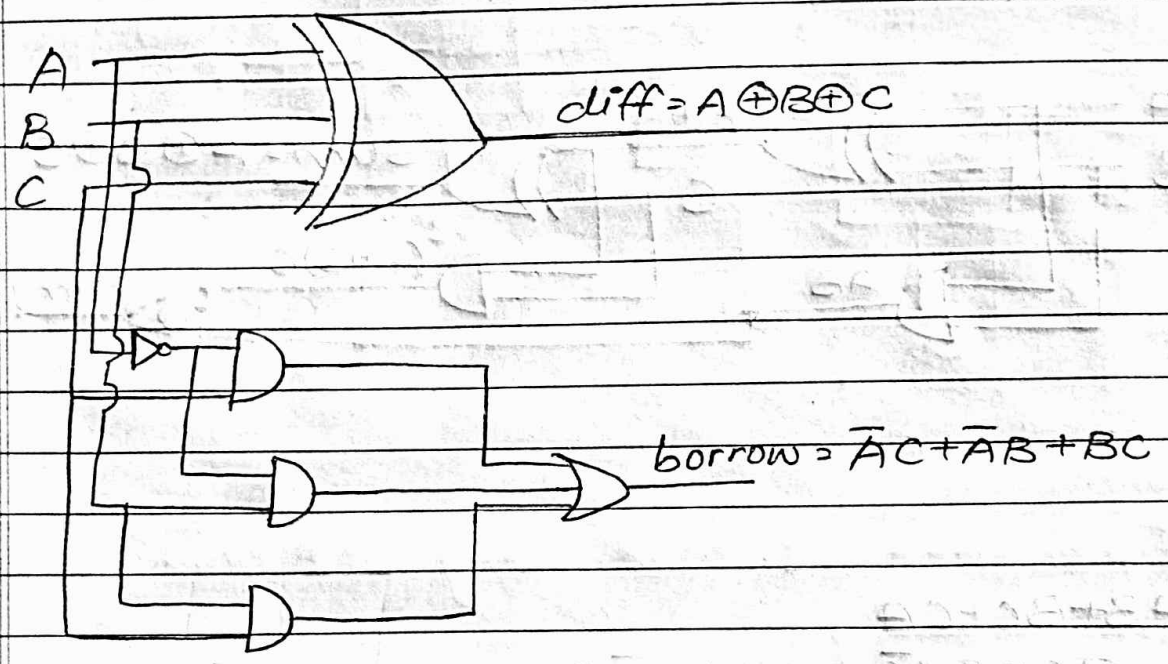
$$\text{borrow} = \bar{A}C + \bar{A}B + BC$$



Implement full adder using half adder

HA  
 $Sum = A \oplus B$   
 $carry = AB$

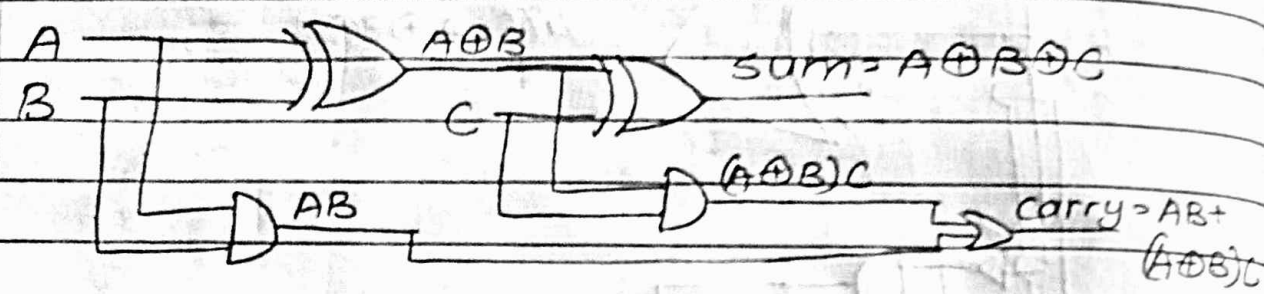FA  
 $sum = A \oplus B \oplus C$   
 $carry = AB + BC + CA$



$$\begin{aligned}
 & AB + BC + CA \\
 &= ABC + AB\bar{C} + A\bar{B}C + \bar{A}BC + ABC + A\bar{B}C \\
 &= ABC + AB\bar{C} + \bar{A}BC + A\bar{B}C \\
 &= AB(C + \bar{C}) + C(\bar{A}B + A\bar{B}) \\
 &= AB + C(A \oplus B)
 \end{aligned}$$

Implement full subtractor using half subtractor

HS


$$\text{diff} = A \oplus B$$

$$\text{borrow} = \bar{A}B$$

FS

$$\text{diff} = A \oplus B \oplus C$$
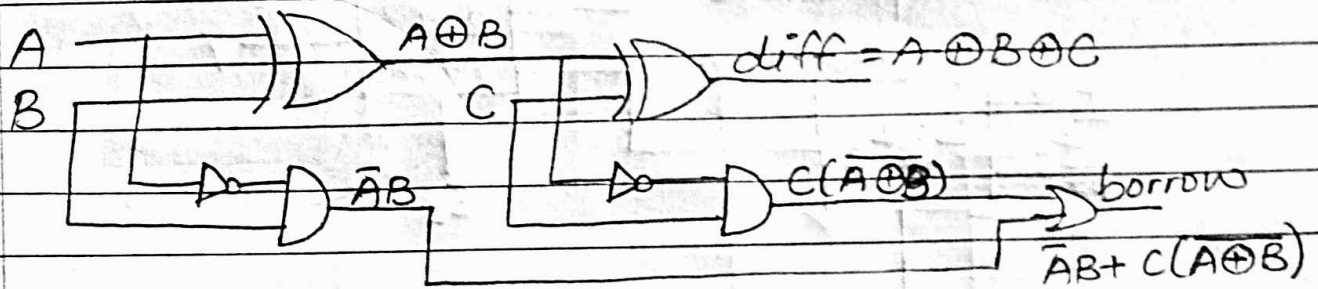
$$\text{borrow} = \bar{A}C + \bar{A}B + BC$$



$$\bar{A}C + \bar{A}B + BC$$

$$\bar{A}BC + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}\bar{B}\bar{C} + ABC + \bar{A}BC$$

$$\bar{A}BC + \bar{A}\bar{B}C + \bar{A}B\bar{C} + ABC + \bar{A}BC$$

$$\bar{A}BC + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$$

$$\bar{A}(BC + B\bar{C}) + C(\bar{A}B + AB)$$


$$\bar{A}B(C + \bar{C}) + C(\bar{A}B + AB)$$

$$\bar{A}B + C(\bar{A}B + AB)$$

MUX Tree


Implement 4:1 MUX using 2:1 MUX

Handwritten scribbles

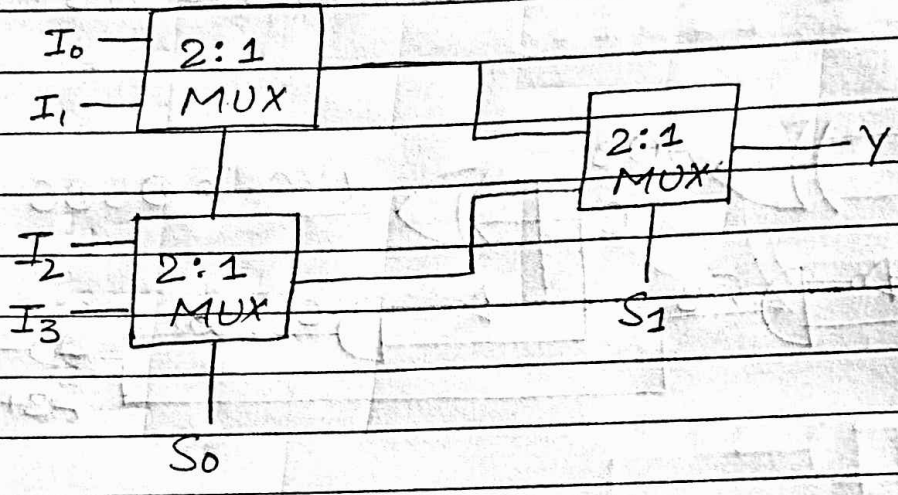

Implement 8:1 MUX using 2:1 MUX


Handwritten scribbles

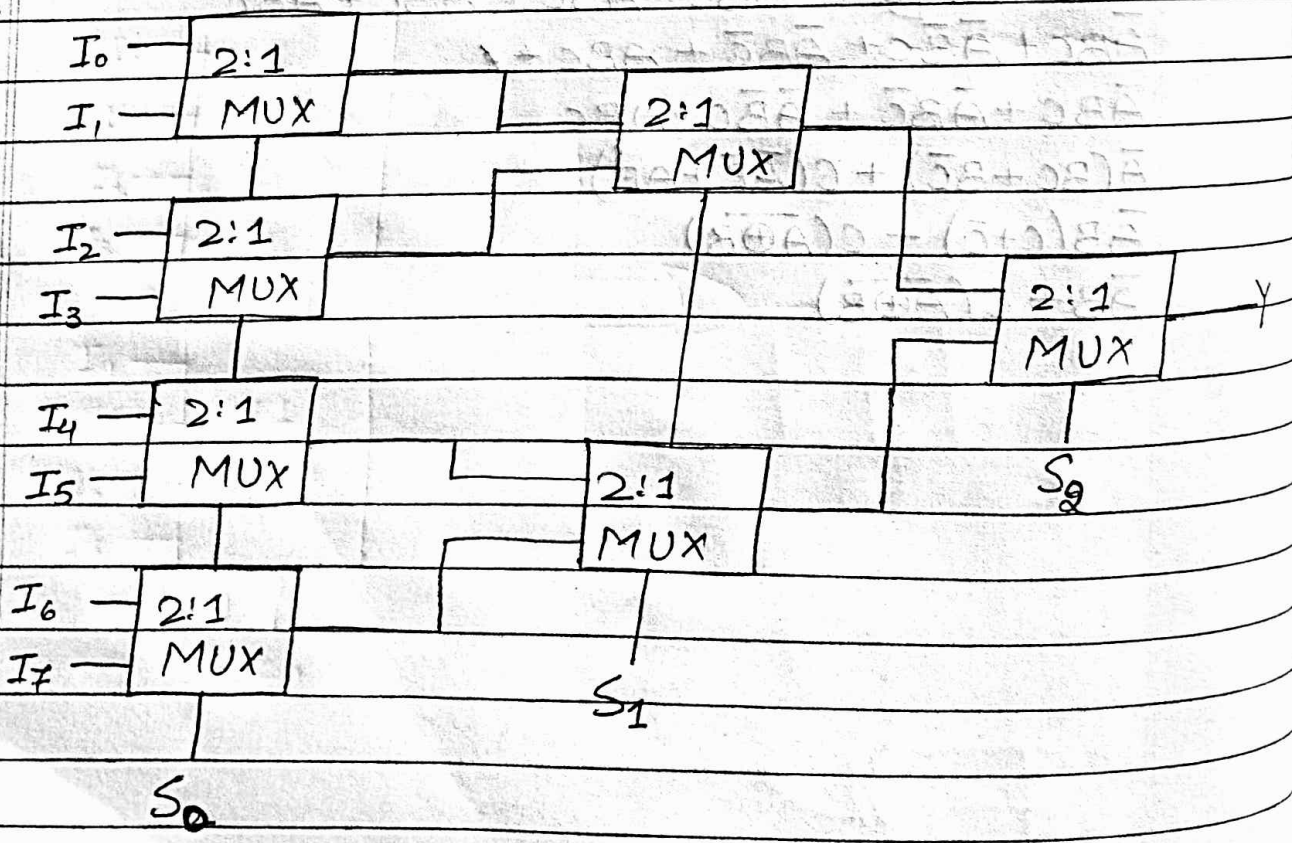







Implement 8:1 using 4:1 MUX

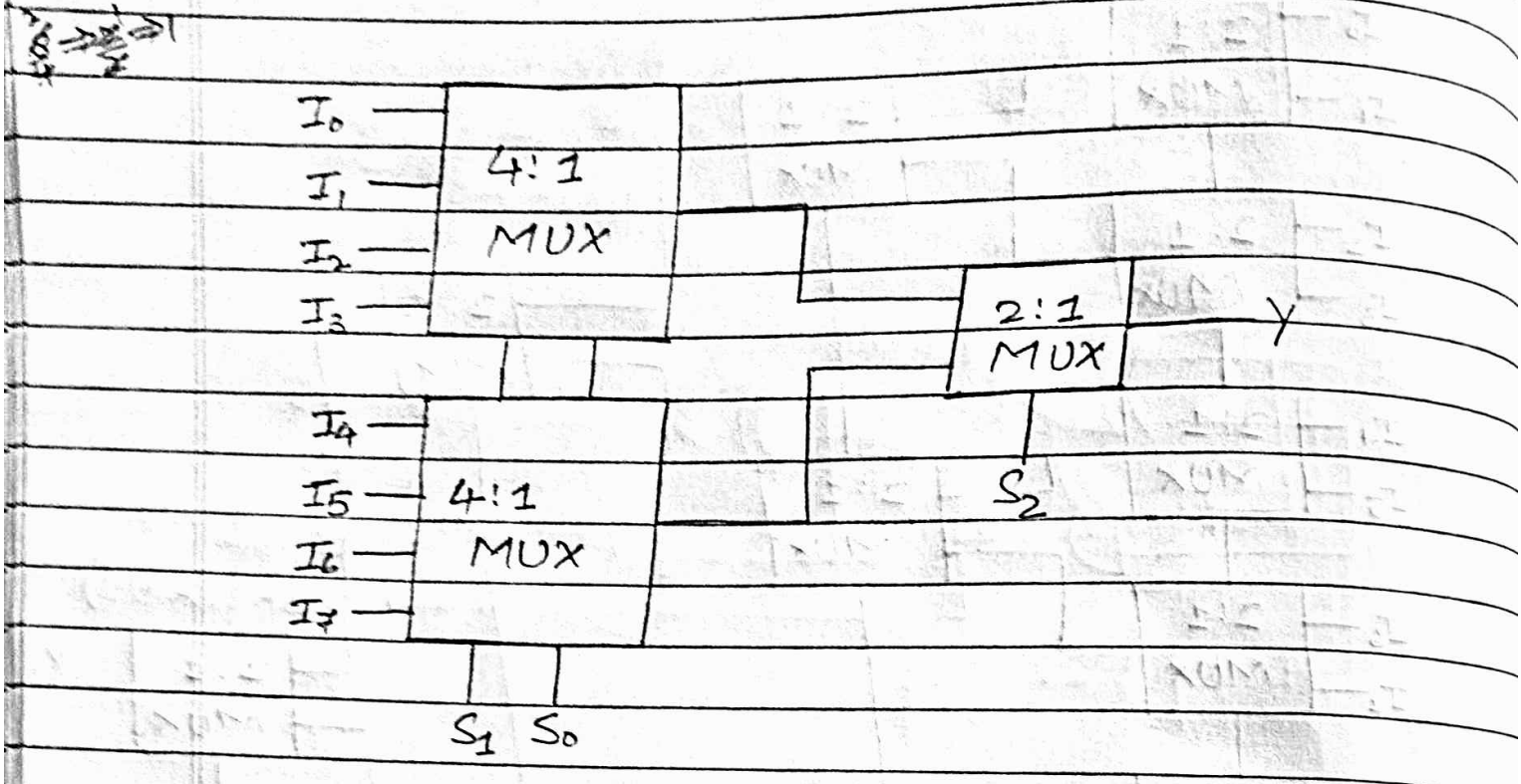


Implement 8:1 using 4:1 MUX and OR Gate only

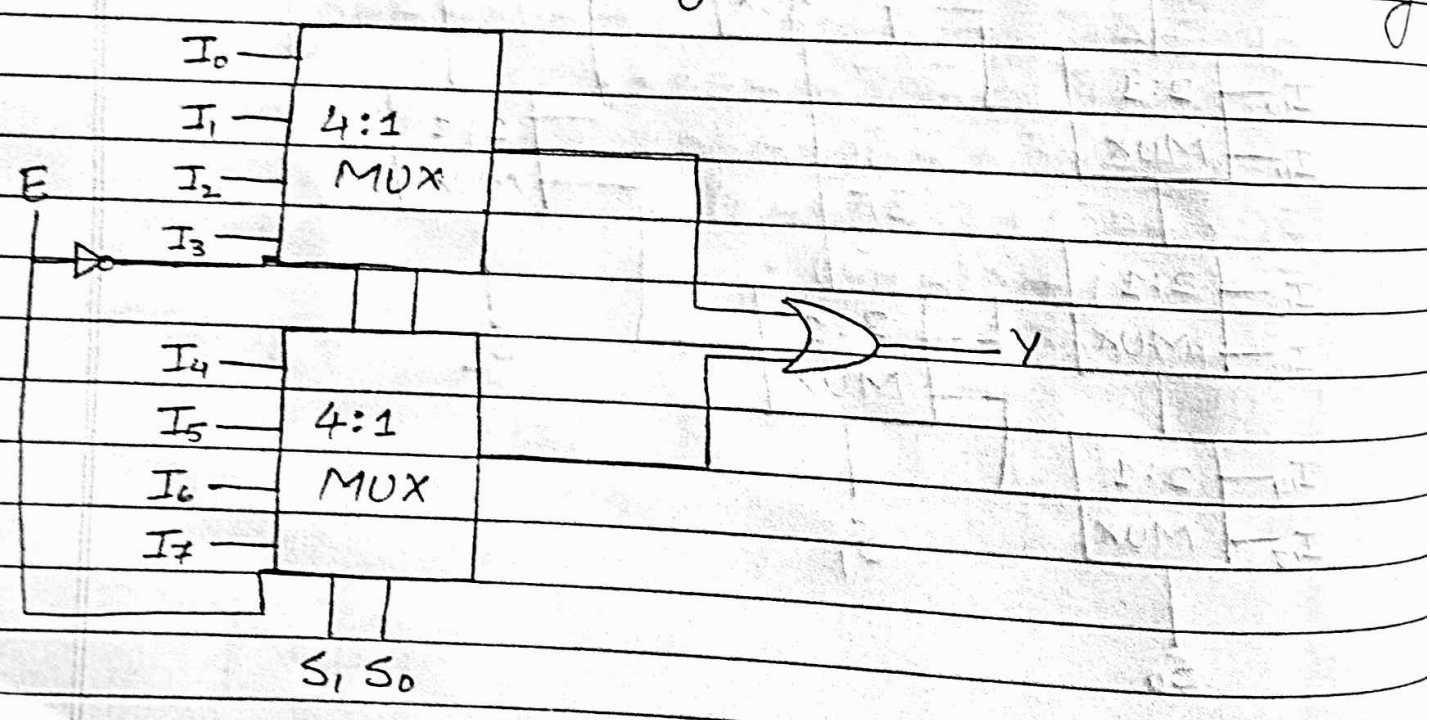

Implement 32:1 using 16:1 MUX

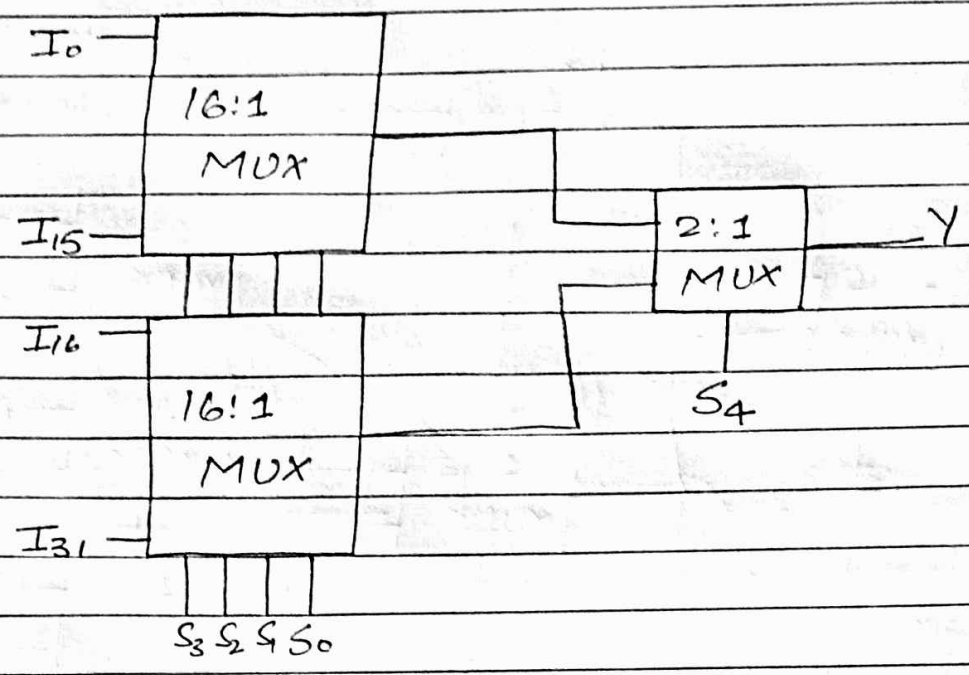


Implement 32:1 using 4:1 MUX

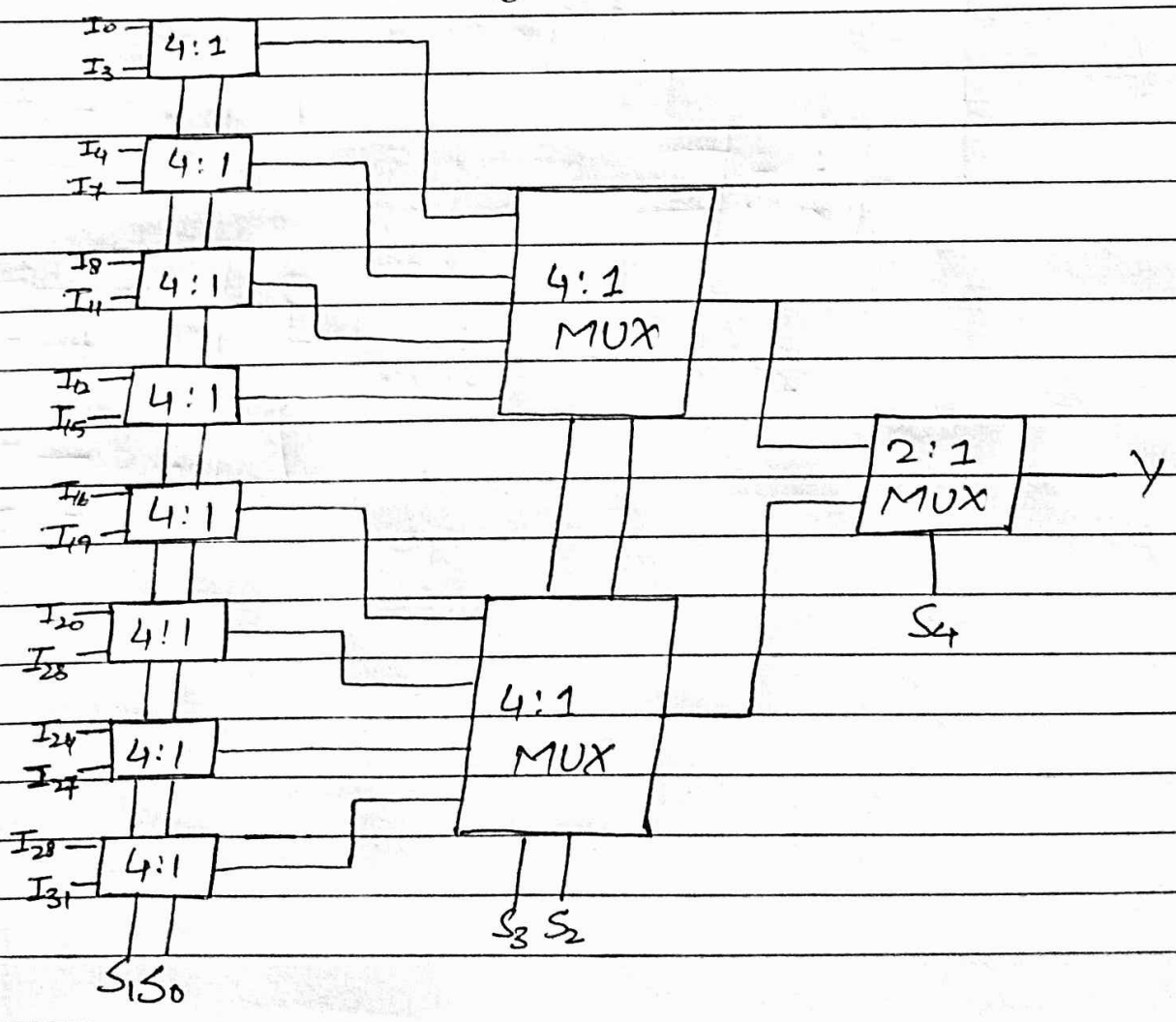

$f(A, B, C) = \sum m(0, 1, 5, 6, 7)$  Implement using 4:1

A \ BC	$I_0$ 00	$I_1$ 01	$I_2$ 10	$I_3$ 11
0	1 <sup>0</sup>	1 <sup>1</sup>	2	3
1	4	1 <sup>5</sup>	1 <sup>6</sup>	1 <sup>7</sup>
	$\bar{A}$	$A + \bar{A}$ 1	A	A

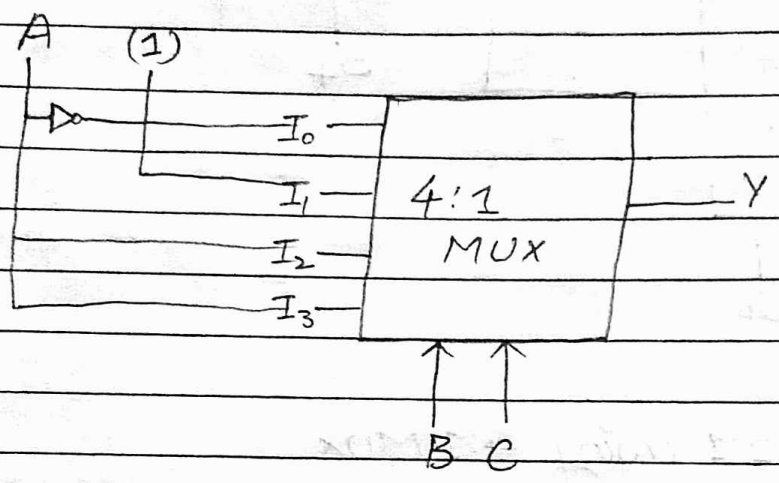4:1  
↓  
2 select lines  
BC → select lines  
A → input





$$f(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$$

Implement using 8:1 MUX


A	BCD								
	000	001	010	011	100	101	110	111	
0	0	1	2	3	4	5	6	7	
1	8	9	10	11	12	13	14	15	
	0	$\bar{A}$	0	1	1	A	A	A	

8:1

↓  
3 select lines

BCD → select lines


A → input

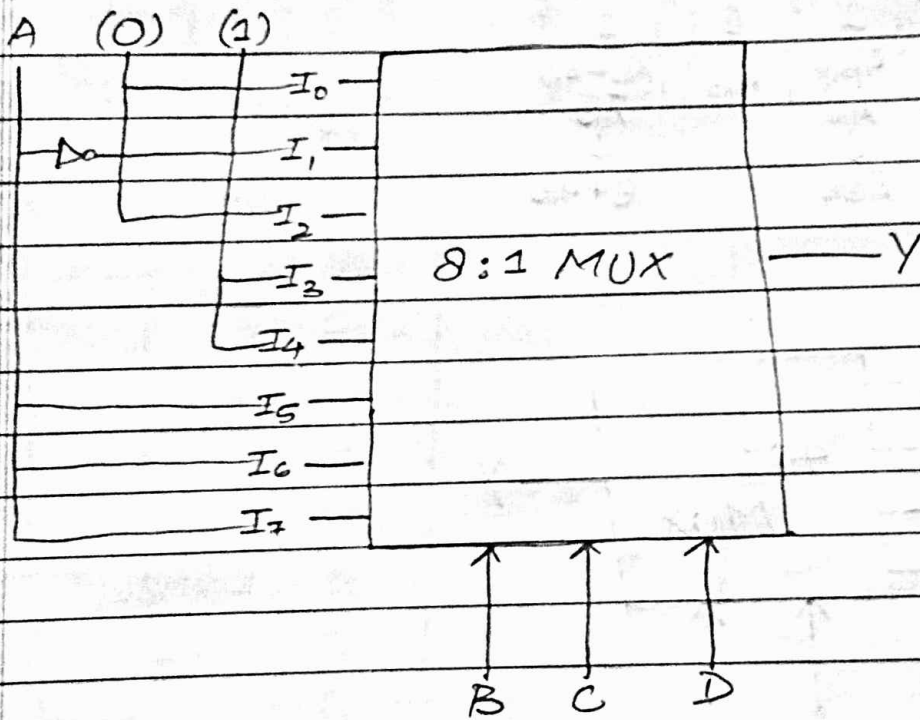

$f(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$  Implement using 4:1 Mux

Select Lines  $\rightarrow$  CD  
input  $\rightarrow$  AB

AB \ CD	$I_0$ 00	$I_1$ 01	$I_2$ 10	$I_3$ 11
00	0	1	2	3
01	4	5	6	7
10	8	9	10	11
11	12	13	14	15
	$\bar{A}B + AB$ $= B$	$\bar{A}\bar{B} + AB$ $= A \oplus B$	$AB$	$\bar{A}\bar{B} + \bar{A}B$ $= \bar{A}$ $\downarrow$ $B + A\bar{B}$

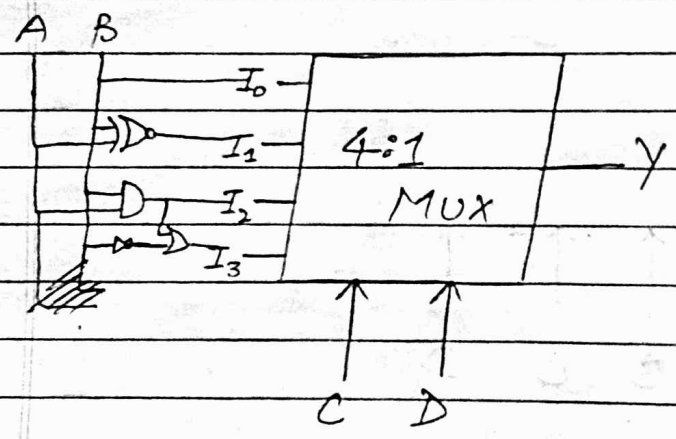


$$f(A, B, C, D) = \sum m(1, 3, 4, 5, 6, 8, 9, 10, 11, 12, 13, 14, 15)$$

using 8:1 MUX



BCD  $\rightarrow$  select lines

A  $\rightarrow$  input

A	BCD 000	001	010	011	100	101	110	111
0	0 <sup>0</sup>	1 <sup>1</sup>	2 <sup>2</sup>	1 <sup>3</sup>	1 <sup>4</sup>	1 <sup>5</sup>	1 <sup>6</sup>	7 <sup>7</sup>
1	1 <sup>8</sup>	1 <sup>9</sup>	1 <sup>10</sup>	1 <sup>11</sup>	1 <sup>12</sup>	1 <sup>13</sup>	1 <sup>14</sup>	1 <sup>15</sup>
	A	1	A	1	1	1	1	A

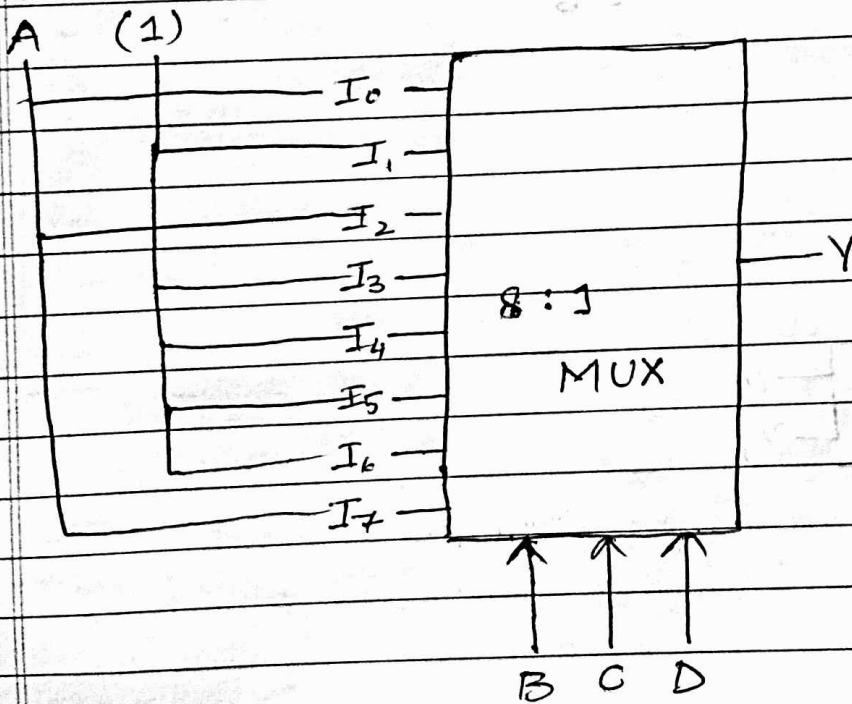


Demux → one to many

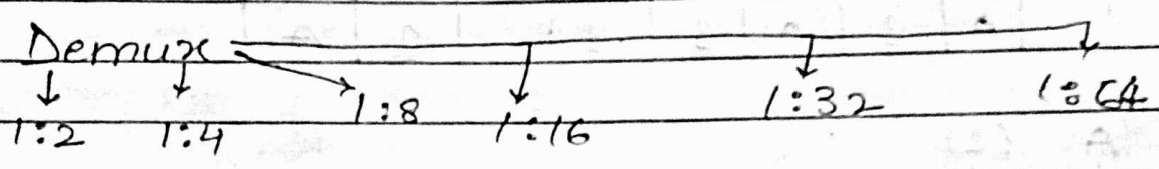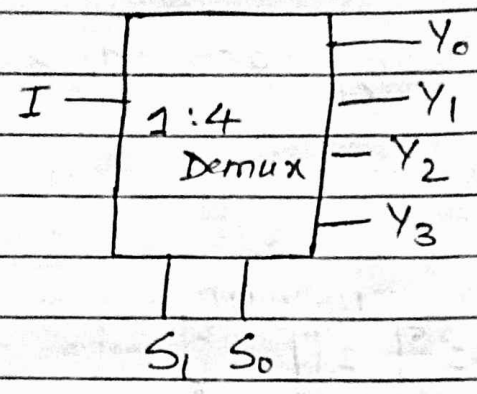

1:2 Demux


I Block diag.

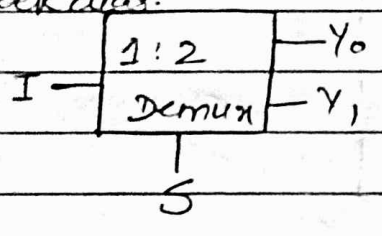

II Truth Table


I	S	Y
I	0	$Y_0 = I\bar{S}$
I	1	$Y_1 = IS$

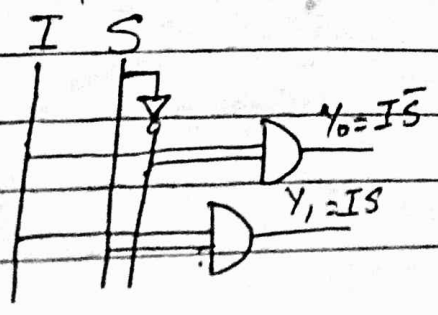III Exp.  $Y_0 = I\bar{S}$        $Y_1 = IS$





## 1:4 Demux

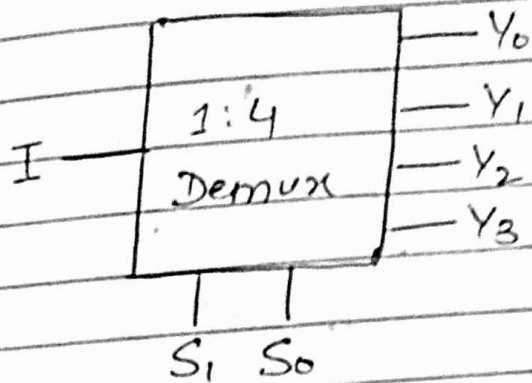

## Truth Table

I	S <sub>1</sub>	S <sub>0</sub>	Y
I	0	0	Y <sub>0</sub>
I	0	1	Y <sub>1</sub>
I	1	0	Y <sub>2</sub>
I	1	1	Y <sub>3</sub>


## Exp.

$$Y_0 = I \bar{S}_1 \bar{S}_0$$


$$Y_1 = I \bar{S}_1 S_0$$

$$Y_2 = I S_1 \bar{S}_0$$

$$Y_3 = I S_1 S_0$$

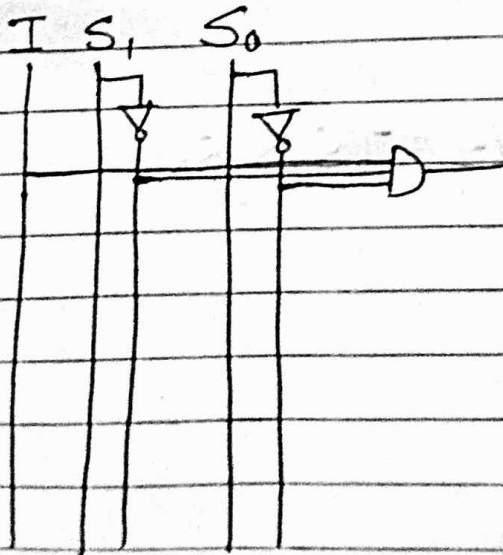

1:8 Demux

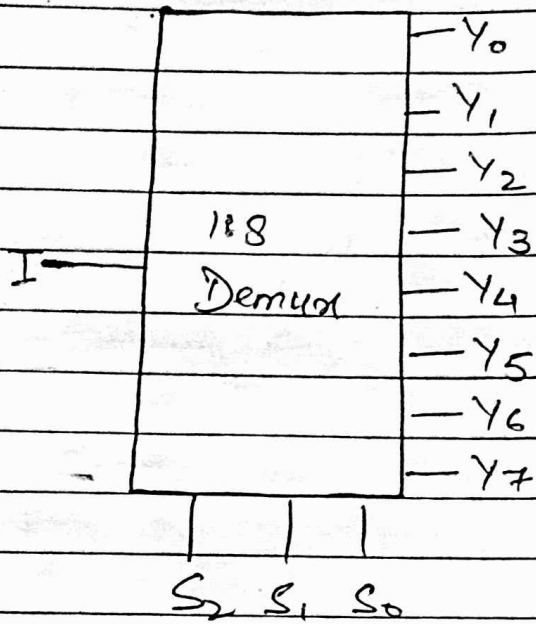

I	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y
I	0	0	0	Y <sub>0</sub>
I	0	0	1	Y <sub>1</sub>
I	0	1	0	Y <sub>2</sub>
I	0	1	1	Y <sub>3</sub>
I	1	0	0	Y <sub>4</sub>
I	1	0	1	Y <sub>5</sub>
I	1	1	0	Y <sub>6</sub>
I	1	1	1	Y <sub>7</sub>

Exp.

$$Y_0 = I \bar{S}_2 \bar{S}_1 \bar{S}_0$$

$$Y_1 = I \bar{S}_2 \bar{S}_1 S_0$$

$$Y_2 = I \bar{S}_2 S_1 \bar{S}_0$$


$$Y_3 = I \bar{S}_2 S_1 S_0$$

$$Y_4 = I S_2 \bar{S}_1 \bar{S}_0$$

$$Y_5 = I S_2 \bar{S}_1 S_0$$

$$Y_6 = I S_2 S_1 \bar{S}_0$$

$$Y_7 = I S_2 S_1 S_0$$

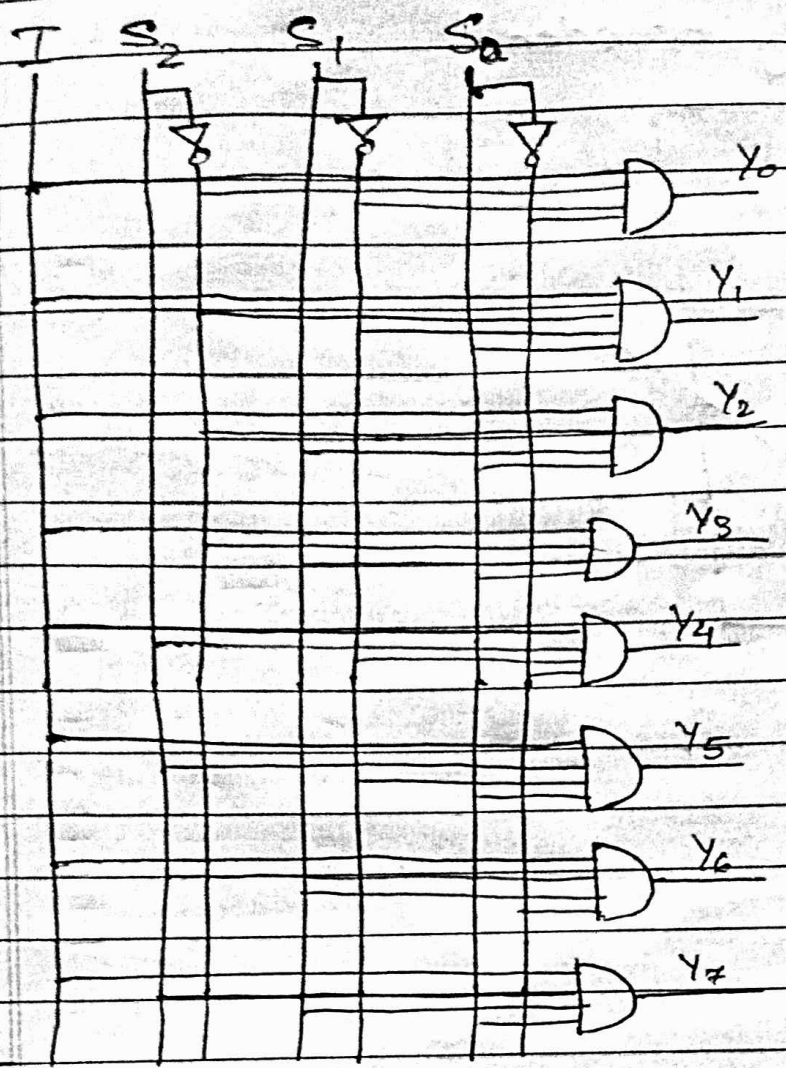

MUX

Many to one

$I/P > O/P$

Select lines are there

8:1

4:1

2:1

Encoder

Many to many

$I/P > O/P$

No select lines

8:3

4:2

2:1

Demux

One to many

$I/P < O/P$

Select lines are there

1:4

1:8

1:16

Decoder

Many to many

$I/P < O/P$

No select lines

2:4


3:8





# Encoder [4:2]

I

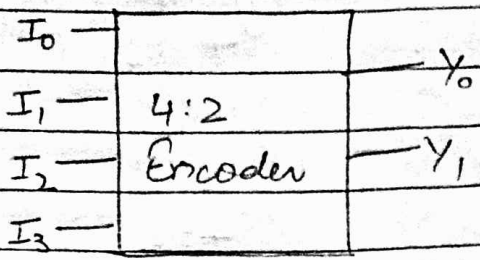

## II Truth Table


$I_0$	$I_1$	$I_2$	$I_3$	$Y_1$	$Y_0$
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

## III Expression


$$Y_0 = I_1 + I_3$$

$$Y_1 = I_2 + I_3$$

IV

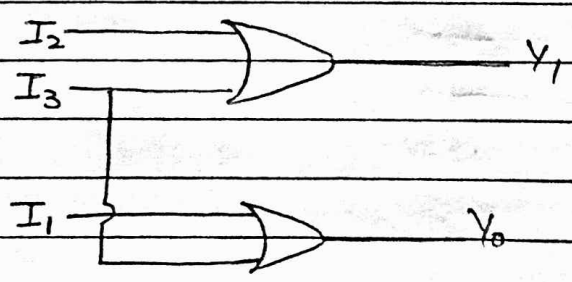

# Encoder [8:3]

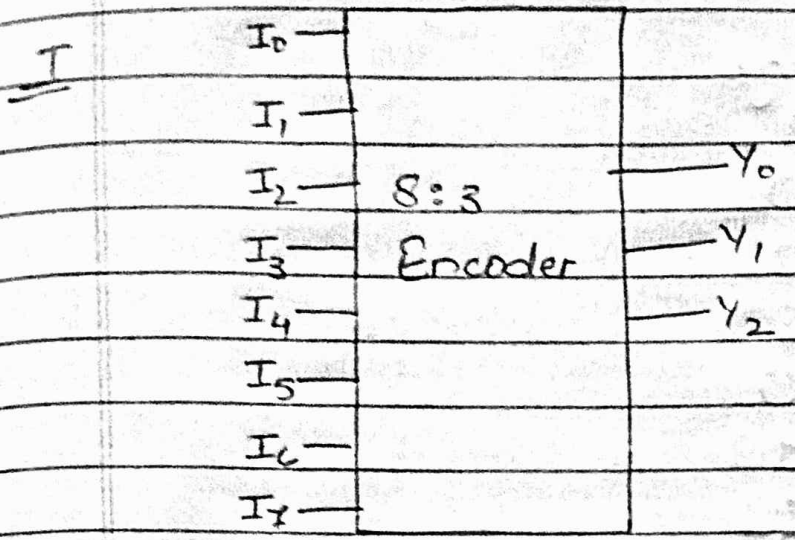

## II Truth Table




$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$	$Y_2$	$Y_1$	$Y_0$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

## III Expression

$$Y_2 = I_4 + I_5 + I_6 + I_7$$

$$Y_1 = I_2 + I_3 + I_6 + I_7$$


$$Y_0 = I_1 + I_3 + I_5 + I_7$$

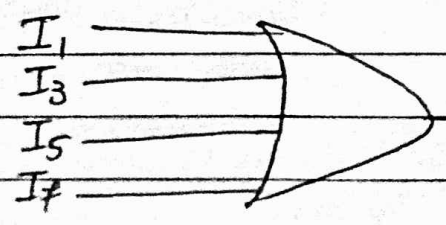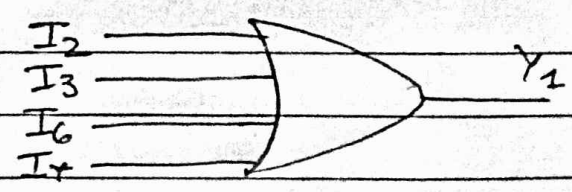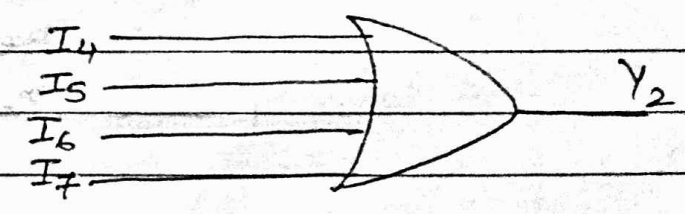

Implement full adder using 3:8 Decoder

A	B	C	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

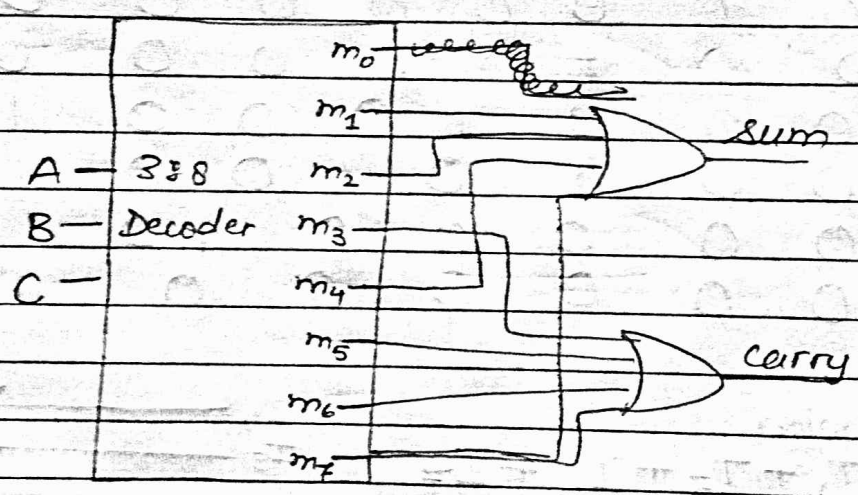$sum = m_1 + m_2 + m_4 + m_7$   
 $carry = m_3 + m_5 + m_6 + m_7$






Implement half adder on 2:4 decoder

A	B	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

sum =  $m_1 + m_2$   
 carry =  $m_3$

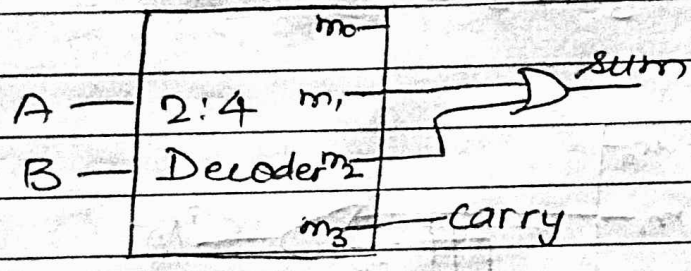




Implement full subtractor using 3:8 Decoder

A	B	C	diff	borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\text{diff} = m_1 + m_2 + m_4 + m_7$$

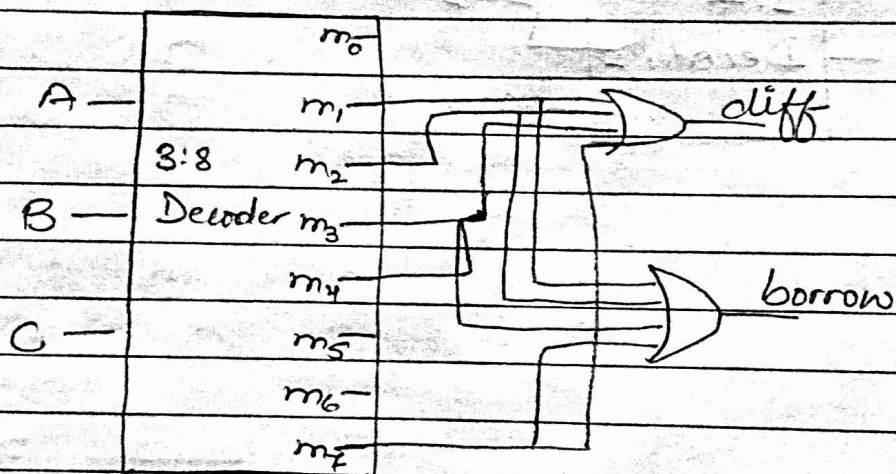
$$\text{borrow} = m_1 + m_2 + m_3 + m_7$$



Implement Half subtractor using 2:4 Decoder

A	B	diff	borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$diff = m_1 + m_2$   
 $borrow = m_1$

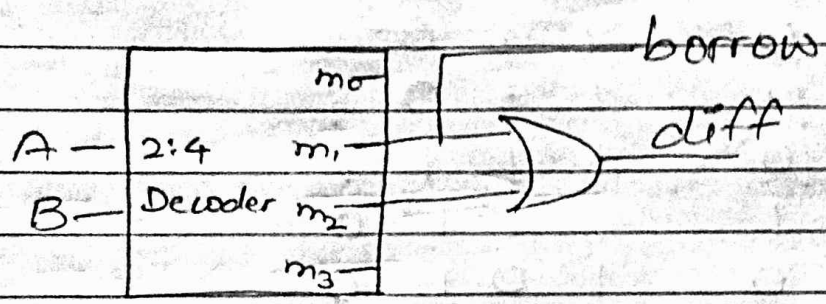

Code Converter

Binary to Gray

<u>T</u>	B <sub>0</sub>	B <sub>1</sub>	B <sub>2</sub>	B <sub>3</sub>	G <sub>0</sub>	G <sub>1</sub>	G <sub>2</sub>	G <sub>3</sub>
	0	0	0	0	0	0	0	0
	0	0	0	1	0	0	0	1
	0	0	1	0	0	0	1	1
	0	0	1	1	0	0	1	0
	0	1	0	0	0	1	1	0
	0	1	0	1	0	1	1	1
	0	1	1	0	0	1	0	1
	0	1	1	1	0	1	0	0
	1	0	0	0	1	1	0	0
	1	0	0	1	1	1	0	1
	1	0	1	0	1	1	1	1
	1	0	1	1	1	1	1	0
	1	1	0	0	1	0	1	0
	1	1	0	1	1	0	1	1
	1	1	1	0	1	0	0	1
	1	1	1	1	1	0	0	0

II  $G_0 = \sum m(8, 9, 10, 11, 12, 13, 14, 15)$

	B <sub>2</sub>	B <sub>3</sub>	00	01	11	10	
B <sub>0</sub> B <sub>1</sub>			0	1	3	2	
			4	5	7	6	
			12	13	15	14	→ B <sub>0</sub>
			8	9	11	10	

$G_0 = B_0$



$$G_1 = \sum m(4, 5, 6, 7, 8, 9, 10, 11)$$

$B_2 B_1$ \ $B_2 B_1$	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

$$G_1 = \bar{B}_0 B_1 + B_0 \bar{B}_1 = B_0 \oplus B_1$$

$$G_2 = \sum m(2, 3, 4, 5, 10, 12, 13, 14)$$

$B_2 B_1$ \ $B_2 B_1$	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

$$G_2 = B_1 \bar{B}_2 + \bar{B}_1 B_2 = B_1 \oplus B_2$$

$$G_3 = \sum m(1, 2, 5, 6, 9, 10, 13, 14)$$


$B_2 B_1$ \ $B_2 B_1$	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

$$G_3 = \bar{B}_2 B_3 + B_2 \bar{B}_3 = B_2 \oplus B_3$$



# ~~Gray to Binary~~

Realization :-

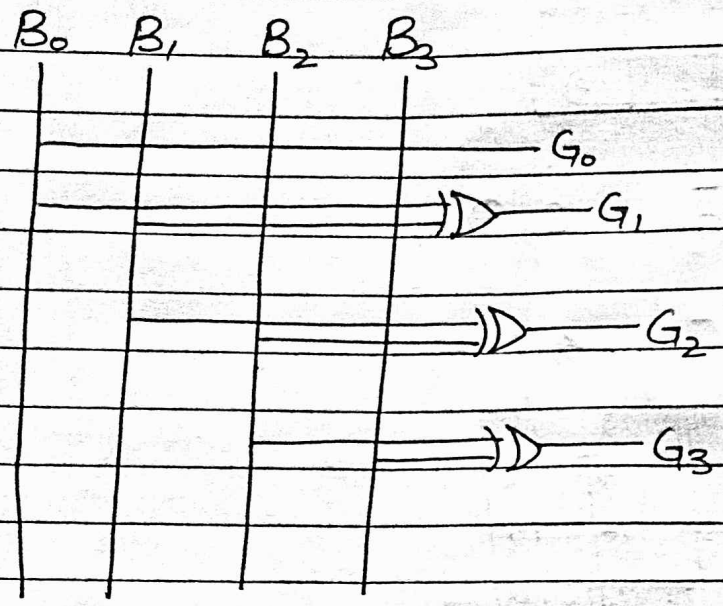

## Gray to Binary

G <sub>0</sub>	G <sub>1</sub>	G <sub>2</sub>	G <sub>3</sub>	B <sub>0</sub>	B <sub>1</sub>	B <sub>2</sub>	B <sub>3</sub>
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
1	0	0	0	1	1	1	1
1	0	0	1	1	1	1	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	0	1	0	1	1
1	1	1	1	1	0	1	0

$$B_0 = \sum m(8, 9, 10, 11, 12, 13, 14, 15)$$

$G_2 G_1$ \ $G_2 G_1$	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

$$B_0 = G_0$$

$$B_1 = \sum m(4, 5, 6, 7, 8, 9, 10, 11)$$

$G_2 G_1$ \ $G_2 G_1$	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

$$B_1 = \bar{G}_0 G_1 + G_0 \bar{G}_1 = G_0 \oplus G_1$$

$$B_2 = \sum m(2, 3, 4, 5, 8, 9, 14, 15)$$

$G_2 G_1$ \ $G_2 G_1$	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

$$\begin{aligned} B_2 &= \bar{G}_0 \bar{G}_1 G_2 + \bar{G}_0 G_1 \bar{G}_2 + G_0 \bar{G}_1 G_2 + G_0 G_1 \bar{G}_2 \\ &= \bar{G}_0 (\bar{G}_1 G_2 + G_1 \bar{G}_2) + G_0 (G_1 G_2 + \bar{G}_1 \bar{G}_2) \\ &= \bar{G}_0 (G_1 \oplus G_2) + G_0 (G_1 \oplus G_2) \end{aligned}$$

Comparator [2 inputs 3 outputs]  $\rightarrow$  [1 would be high]

A —	1 bit	— A < B
		— A > B
B —		— A = B

(A <sub>1</sub> A <sub>0</sub> ) A —	2-bit	— A < B
		— A > B
(B <sub>1</sub> B <sub>0</sub> ) B —		— A = B


(A <sub>2</sub> A <sub>1</sub> A <sub>0</sub> ) A —	3-bit	— A < B
		— A > B
(B <sub>2</sub> B <sub>1</sub> B <sub>0</sub> ) B —		— A = B

Types of comparator

- Identity  $\rightarrow$  Two values [only one input] one output
- Magnitude  $\rightarrow$  Two input, 3 output



# 1-Bit Comparator

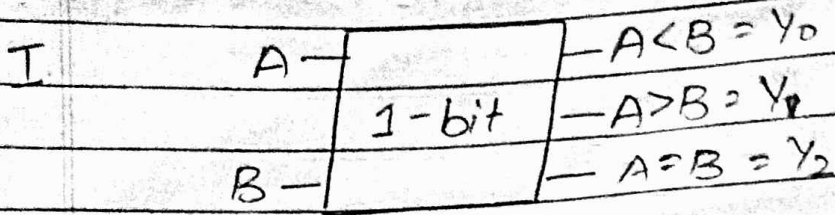

II Truth Table

	A	B	$Y_0$ A < B	$Y_1$ A > B	$Y_2$ A = B
0	0	0	0	0	1
1	0	1	1	0	0
2	1	0	0	1	0
3	1	1	0	0	1

III  $Y_0 = \bar{A}B$


A \ B	0	1
0	0	1
1	2	3

+  $\bar{A}B$

$Y_1 = A\bar{B}$

$Y_2 = \bar{A}\bar{B} + AB = \overline{A \oplus B} = A \odot B$

A \ B	0	1
0	1	0
1	2	3

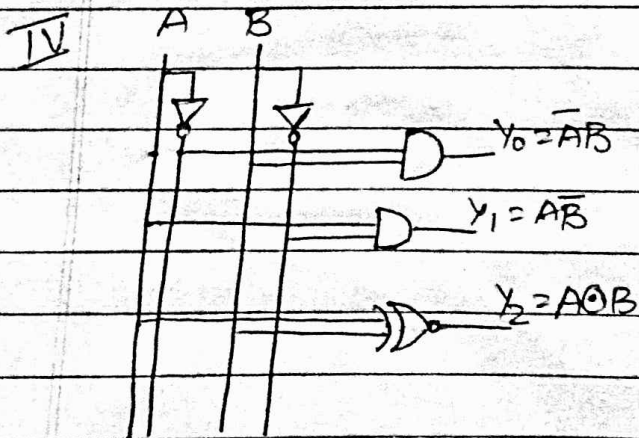



2-bit

<u>I</u>	$(A_1 A_0) A$ —		— $A < B = Y_0$
		2-bit	— $A > B = Y_1$
	$(B_1 B_0) B$ —		— $A = B = Y_2$

II Truth Table

$A_1$	$A_0$	$B_1$	$B_0$	$Y_0$ $A < B$	$Y_1$ $A > B$	$Y_2$ $A = B$
0	0	0	0	0	0	1
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	1	0
0	1	0	1	0	0	1
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	0
1	0	1	0	0	0	1
1	0	1	1	0	0	0
1	1	0	0	0	1	0
1	1	0	1	0	1	0
1	1	1	0	0	1	0
1	1	1	1	0	0	1

III  $Y_0 = \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0$

	$B_1 B_0$	00	01	11	10
$A_1 A_0$	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

$Y_0 \uparrow$

$\bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0$

$Y_1 \uparrow$

	$B_1 B_0$	00	01	11	10
$A_1 A_0$	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10


$Y_1 \uparrow$

$A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_0$

$Y_2 \uparrow$


	$B_1 B_0$	00	01	11	10
$A_1 A_0$	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

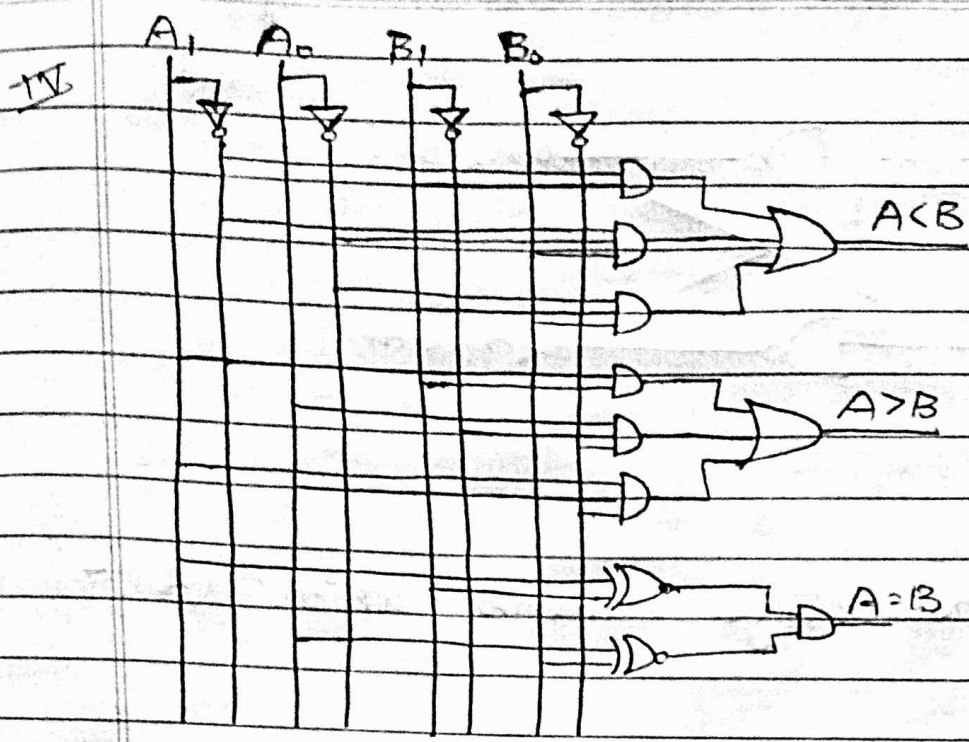$\bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_1 B_0 + A_1 A_0 B_1 B_0 + A_1 \bar{A}_0 B_1 \bar{B}_0$   
 $\bar{A}_1 \bar{B}_1 (\bar{A}_0 \bar{B}_0 + A_0 B_0) + A_1 B_1 (A_0 B_0 + \bar{A}_0 \bar{B}_0)$   
 $(\bar{A}_1 \bar{B}_1 + A_1 B_1) (\bar{A}_0 \bar{B}_0 + A_0 B_0)$   
 $(A_1 \odot B_1) (A_0 \odot B_0)$





# Flip flops SR

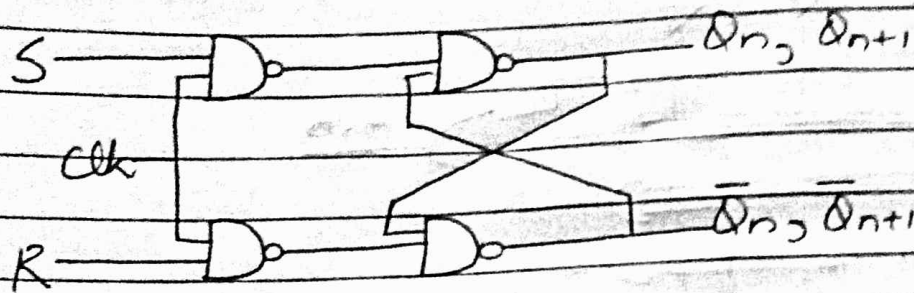

→ latches are basic storage elements which operates at signal levels

## Characteristic Table

clk	S	R	$Q_n$	$Q_{n+1}$	
↑	0	0	0	0	No change
↑	0	0	1	1	
↑	0	1	0	0	Reset
↑	0	1	1	0	
↑	1	0	0	1	Set
↑	1	0	1	1	
↑	1	1	0	X	Invalid Case
↑	1	1	1	X	

## Excitation table

$Q_n$	$Q_{n+1}$	S	R	S	R	$Q_n$	$Q_{n+1}$	S	R
0	0	0	0	0	X	0	0	0	X
0	1	1	0	1	0	0	1	1	0
1	0	0	1	0	1	1	0	0	1
1	1	0	0	X	0	1	1	X	0




Exmp


S \ RQn	00	01	11	10
0	0	1	1	1
1	1	1	X	X

$$Q_{n+1} = S + \bar{R}Q_n$$

Realization

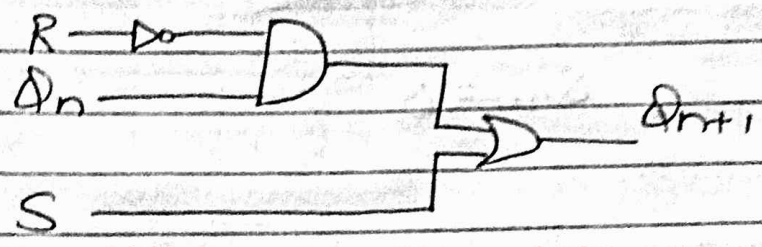

D-Flip Flop

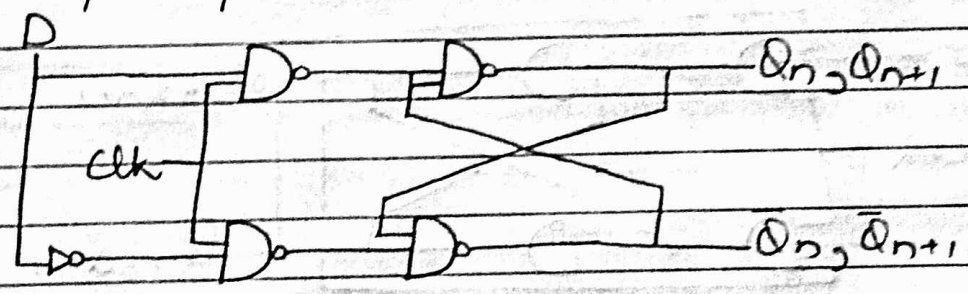

Characteristic Table

clk	D	Q <sub>n</sub>	Q <sub>n+1</sub>	
↑	0	0	0	Reset
↑	0	1	0	
↑	1	0	1	Set
↑	1	1	1	

### Excitation Table

$Q_n$	$Q_{n+1}$	$D$
0	0	0
0	1	1
1	0	0
1	1	1


### Exp

$D$ \ $Q_n$	0	1
0	0	1
1	1	1

$$Q_{n+1} = D$$



### JK - Flip Flop

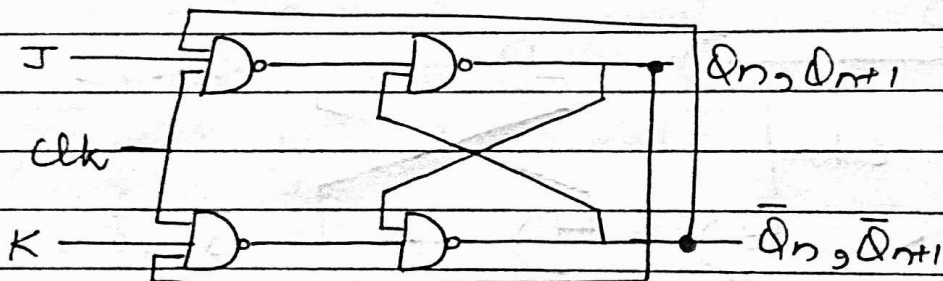

### Characteristic Table

clk	J	K	$Q_n$	$Q_{n+1}$	
↑	0	0	0	0	No change
↑	0	0	1	1	
↑	0	1	0	0	Reset
↑	0	1	1	0	
↑	1	0	0	1	Set
↑	1	0	1	1	
↑	1	1	0	1	Toggle
↑	1	1	1	0	

### Excitation Table

$Q_n$	$Q_{n+1}$	J	K	J	K
0	0	0	0	0	x
0	1	1	0	1	x
1	0	0	1	x	1
1	1	0	0	x	0


$Q_n$	$Q_{n+1}$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Exp



J \ K	0	1
0	0	1
1	1	1

J \ K	0	1
0	0	1
1	1	1

$$Q_{n+1} = \bar{K}Q_n + J\bar{Q}_n$$

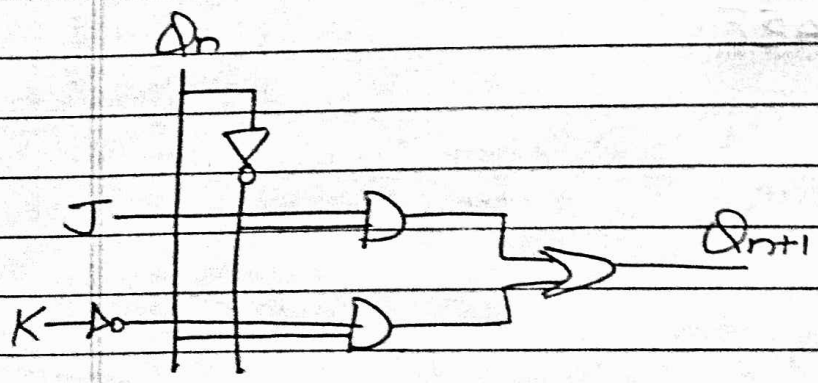

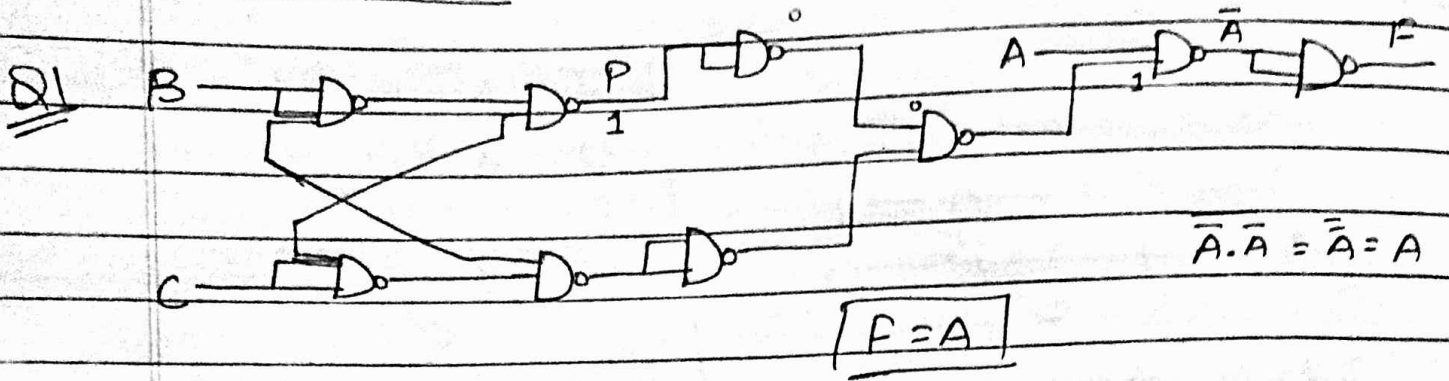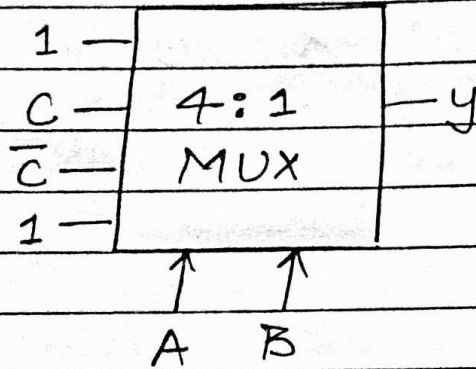

Practice QuestionsQ2

I	A	B	Y
1	0	0	$\bar{A}\bar{B}$
C	0	1	$\bar{A}BC$
$\bar{C}$	1	0	$A\bar{B}\bar{C}$
1	1	1	AB

$$\bar{A}\bar{B} + AB + \bar{A}BC + A\bar{B}\bar{C}$$


$$\bar{A}(\bar{B} + BC) + AB + A\bar{B}\bar{C}$$

$$\bar{A}(\bar{B} + B)(\bar{B} + C) + AB + A\bar{B}\bar{C}$$

$$\bar{A}\bar{B} + \bar{A}C + AB + A\bar{B}\bar{C}$$



# T-Flip Flop

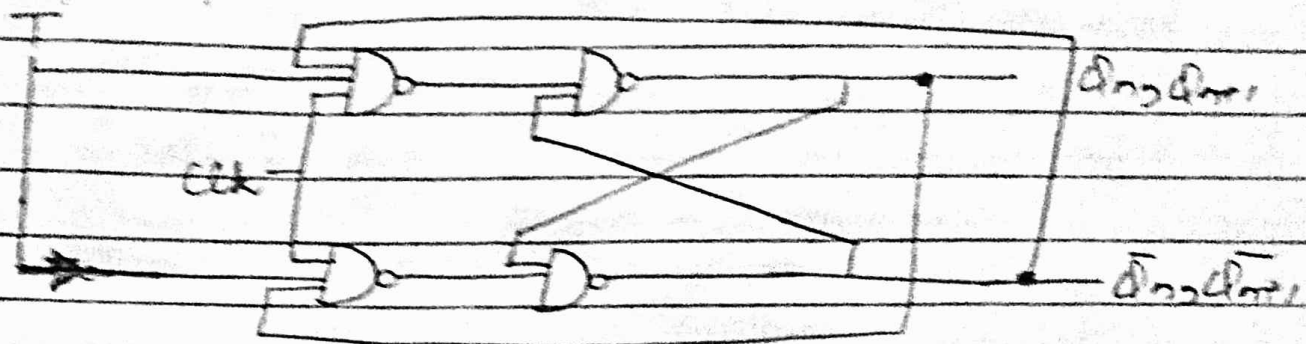

## Characteristic Table

clk	T	Qn	Qn+1	
↑	0	0	0	No change
↑	0	1	1	
↑	1	0	1	Toggle
↑	1	1	0	

## Excitation Table

Qn	Qn+1	T
0	0	0
0	1	1
1	0	1
1	1	0

Exp	T / Qn	
	0	1
0	0	1
1	1	0

$$Q_{n+1} = \bar{T}Q_n + T\bar{Q}_n$$

## Realization



# Conversion of Flip Flop JK to D

① Given  $\rightarrow$  Excitation table

$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

② Req  $\rightarrow$  Characteristic table

D	$Q_n$	$Q_{n+1}$
0	0	0
0	1	0
1	0	1
1	1	1

③ Combine step ① and ②

D	$Q_n$	$Q_{n+1}$	J	K
0	0	0	0	X
0	1	0	X	1
1	0	1	1	X
1	1	1	X	0


④ Note:  $Q_{n+1}$  don't use after step ③

D	$Q_n$	0	1
0	0	0	X <sup>1</sup>
1	0	X <sup>2</sup>	X <sup>3</sup>

$J = D$

D	$Q_n$	0	1
0	0	X <sup>0</sup>	X <sup>1</sup>
1	0	X <sup>2</sup>	X <sup>3</sup>

$K = \bar{D}$

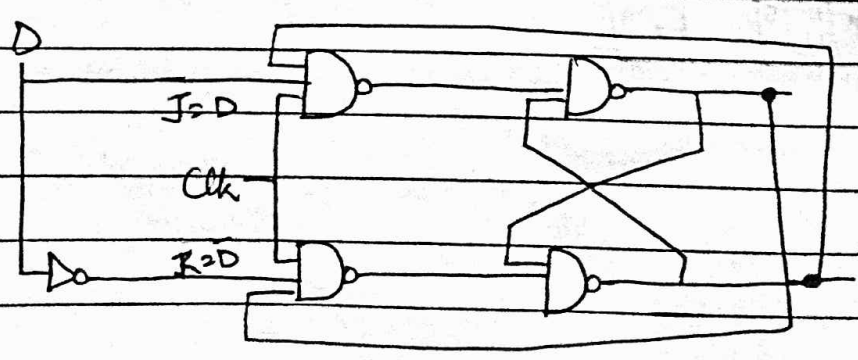

D to JK

Given

Req.

$\bar{Q}_n$	$Q_n$	D	J	K	$\bar{Q}_n$	$Q_n$
0	0	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	1	0	0
1	1	1	0	1	1	0
			1	0	0	1
			1	0	1	1
			1	1	0	1
			1	1	1	0

Combine

J	K	$\bar{Q}_n$	$Q_n$	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

J \ $\bar{Q}_n$	00	01	11	10
0	0	1	1	2
1	1	1	1	1

$$D = \bar{K}\bar{Q}_n + J\bar{Q}_n$$





### SR to JK

#### SR Excitation Table

$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

#### JK Charac Table

CLK	J	K	$Q_n$	$Q_{n+1}$
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

#### Combine -

J	K	$Q_n$	$Q_{n+1}$	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	0	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

Exp for S:-


	$KQ_n$			
$J$	00	01	10	11
0	0 <sup>0</sup>	X <sup>1</sup>	3 <sup>3</sup>	2 <sup>2</sup>
1	1 <sup>4</sup>	X <sup>5</sup>	7 <sup>7</sup>	1 <sup>6</sup>

$S = J\bar{Q}_n$

Exp for R:-

	$KQ_n$			
$J$	00	01	11	10
0	X <sup>0</sup>	1 <sup>1</sup>	1 <sup>2</sup>	X <sup>2</sup>
1	4 <sup>4</sup>	5 <sup>5</sup>	1 <sup>7</sup>	6 <sup>6</sup>

$R = KQ_n$

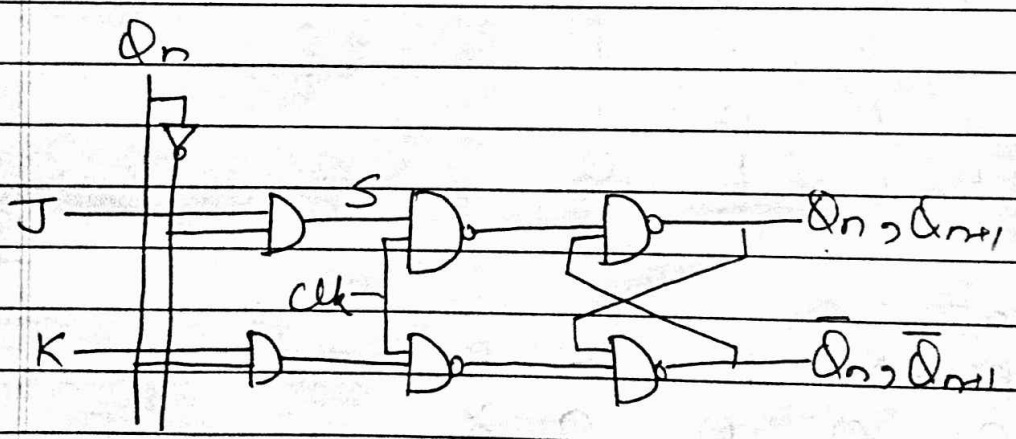

### SR to D

#### SR Excitation Table

$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

#### D Charac Table

Clk	D	$Q_n$	$Q_{n+1}$
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


#### Combining

D	$Q_n$	$Q_{n+1}$	S	R
0	0	0	0	X
0	1	0	0	1
1	0	1	1	0
1	1	1	X	0

#### Exp for D

	$Q_n$	0	1	
D	0	0	1	$S = D$
	1	1	X	


	$Q_n$	0	1	
D	0	X	1	$R = \bar{D}$
	1	2	3	

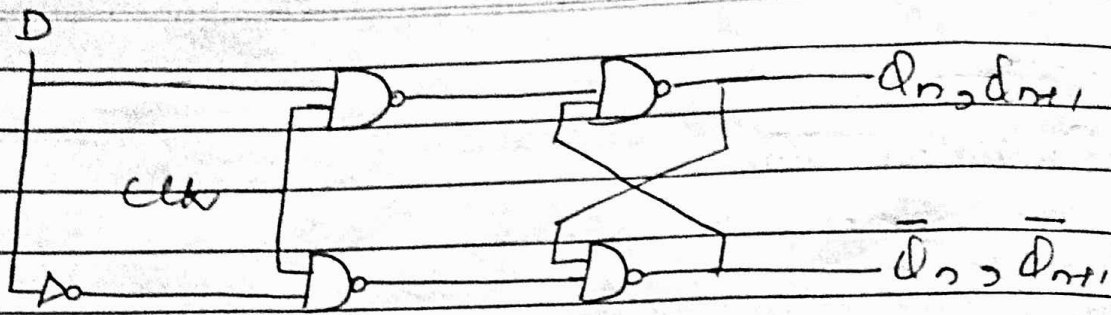





### Master Slave JK Flip Flop

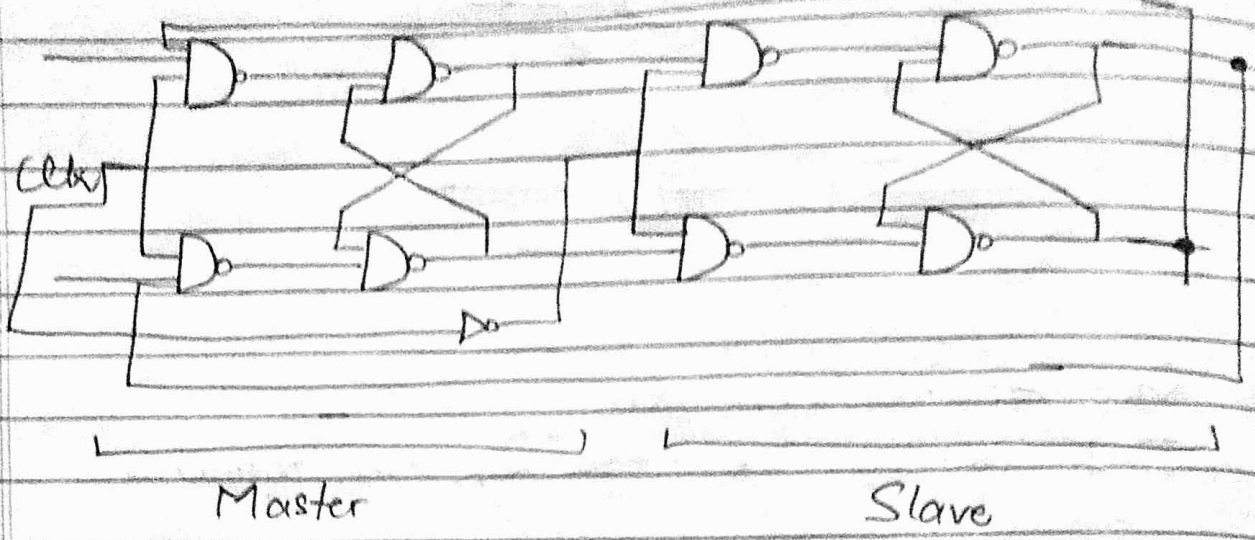

Master


Slave

Practice Ques

$f(A, B, C, D) = \sum m(1, 3, 5, 6, 9, 10, 11, 12, 13, 14)$

using  
4:1 MUX

AB \ CD	I <sub>0</sub>	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>
	00	01	10	11
00	0	1	2	3
01	4	5	6	7
10	8	9	10	11
11	12	13	14	15
AB	1	A + $\bar{A}B$	$\bar{B}$	

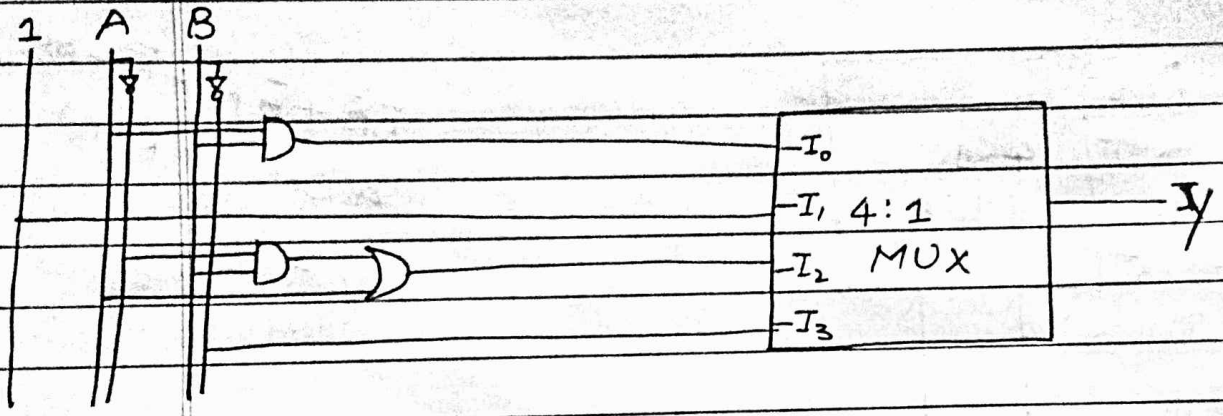

$\Sigma m(1, 3, 5, 6, 9, 10, 11, 12, 13, 14)$  using 8:1 MUX

A	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$
0	0	1	2	1	4	1	1	7
1	8	1	1	1	1	1	1	5
	0	1	A	1	A	1	1	0

