

Experiment Title 10

STUDENT NAME: RAJDEEP JAISWAL

UID: 20BCS2761

SECTION: 20BCS26-B

SEMESTER: 02

DATE OF PERFORMANCE: MAY 7, 2021



SUBJECT NAME: BEEE

○ **Aim: To measure gain of non- inverting operational amplifier.**

○ **Apparatus:**

Sr. No.	EQUIPMENT NAME	SPECIFICATIONS AND RANGE	QUANTITY IN No.
1.	Op-amp IC	IC 741 op-amp	1
2.	CRO	230 V, 30 MHZ	1
3.	Resistor	10 kilo ohms, 1 kilo ohm	2
4.	Digital multimeter	-----	1
5.	Function generators	10 Hz to 1MHz	1
6.	CRO PROBE	-----	2
7.	BREAD BOARD	-----	1
8.	Connecting wires	As per requirement	-----

o Circuit Diagram:

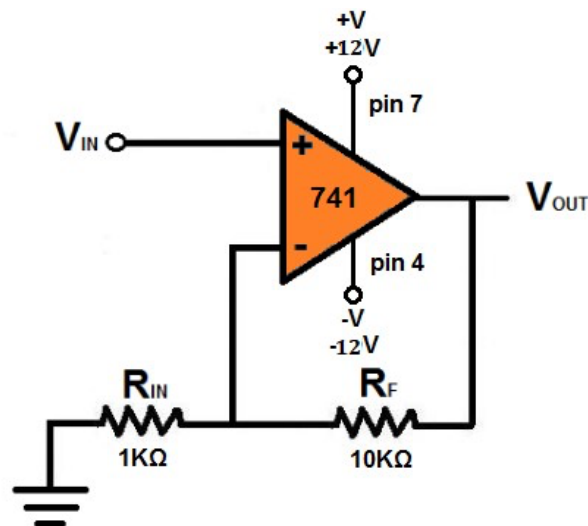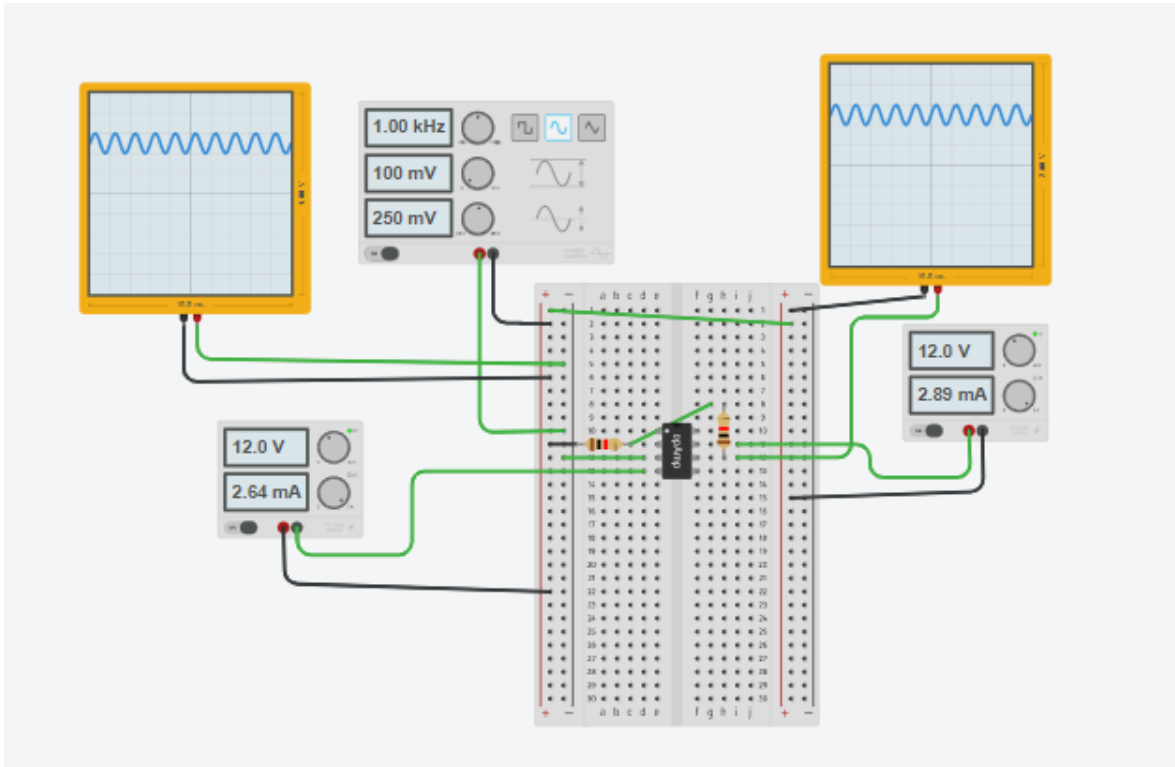

○ THEORY:

Non-inverting Amplifier: An amplifier whose O/P is in phase with the input. It can amplify ac & dc signals. Its gain depends upon the values of feedback resistance (RF) & input resistance (R₁). Figure 1 shows inverting amplifier.

$$V_O = V_{IN} (1 + R_F/R_{in})$$

Gain

$$A = (1 + R_F/R_{in})$$

4. Steps for experiment:

1. Connect the circuit.
2. Connect supply voltage to I/P.
3. Note the values of RF & R₁.
4. Note V_{IN} & V_{OUT} with the digital multimeter.
5. Repeat steps 2 & 3 for different values of RF & R₁.

OBSERVATION:

S. No.	R_F	R_{IN}	V_{IN}	V_o	GAIN $1 + R_f/R_{in}$
1	10 KILO OHM	1 KILO OHM	-12 V	-132 V	11

5. Calculations/Theorems /Formulas used etc

$$V_o = (1 + R_f/R_{in}) V_{in}$$

$$V_o = (1 + 10/1) * (-12)$$

$$V_o = 11 * (-12) = -132 \text{ V}$$

$$\text{GAIN (A)} = 1 + R_f/R_{in}$$

$$= 1 + 10/1$$

$$= 11$$

6. Sources of error:

Due to internal resistance of multimeter.


Due to interruption of power supply.

Due to wrong connection of circuit.

7. Percentage error (if any or applicable):

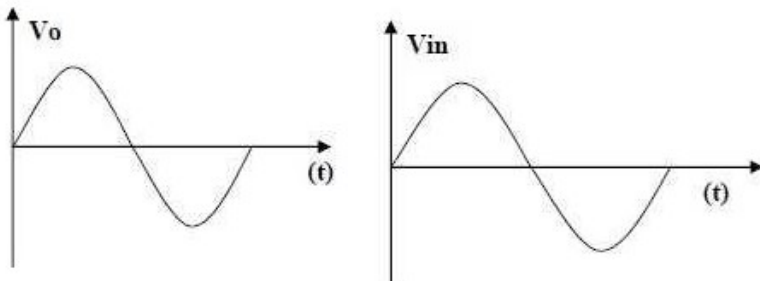8. Result/Output/Writing Summary:

In non-inverting amplifier O/P is in phase with I/P with I/P. The waveform for non-inverting and amplifier:



9. Graphs (If Any): Image /Soft copy of graph paper to be attached here

Learning outcomes (What I have learnt):

From this experiment students will be able to

understand the concept of inverting amplifier

understand the construction and working of inverting amplifier

learn gain of inverting amplifier

Evaluation Grid:

Sr. No.	Parameters	Marks Obtained	Maximum Marks
1.	Worksheet completion including writing learning objectives/Outcomes.(To be submitted at the end of the day).		10
2.	Post Lab Quiz Result.		5
3.	Student Engagement in Simulation/Demonstration/Performance and Controls/Pre-Lab Questions.		5
	Signature of Faculty (with Date):	Total Marks Obtained:	