

## Unit 3: Surprise Test Pool

Hemant Kumar



Final Grade

Submitted late 5/2/21, 2:24 PM (UTC+5:30)

12 / 12

## Assignment Content

 Question 1

1 / 1

An integrator converts a square waveform into

Hide answer choices ^

- A triangular waveform
- B parabola
- C spikes

 Question 2

1 / 1

The IC used in OPAMP is LM 741.

- T True
- F False

 Question 3

1 / 1

An op-amp with negative feedback works as an oscillator. True or false?

- T True
- F False

 Question 4

1 / 1

Current will flow to ground through a virtual ground. True or False?

- T True
- F False

 Question 5

1 / 1

The average value of the two currents flowing into the op-amp input terminals is known as input offset current. True or false?

- T True
- F False



Feedback

## Feedback for student

Your instructor hasn't added feedback

✔ Question 6

1 / 1

An op-amp with positive feedback works as an amplifier. True or false?

- True
- False

✔ Question 7

1 / 1

The inverting op-amp configuration is used as phase shifter. True or false?

- True
- False

✔ Question 8

1 / 1

An integrator converts a square waveform into a triangular waveform. True or false?

- True
- False

✔ Question 9

1 / 1

Which of the following electrical characteristics is not exhibited by an ideal op-amp?

Hide answer choices ^

- A infinite voltage gain
- B zero output resistance
- C zero slew rate
- D infinite bandwidth

✔ Question 10

1 / 1

The common-mode voltage gain is

Hide answer choices ^

- A equal to differential voltage gain
- B greater than differential voltage gain
- C smaller than differential voltage gain

✔ Question 11

1 / 1

In IC LM 741 the pin no. 3 is

Hide answer choices ^

- A inverting
- B output

C non-inverting

D none of above

✔ Question 12

1 / 1

In inverting amplifier output voltage is ..... deg out of phase with input voltage.

Hide answer choices ^

A 90

B 180

C 60

D 120