



BEEE WORKSHEET

EXPERIMENT – 2.3

NAME –

UID –

SEMESTER – 2

CLASS/GROUP –

D.O.P – 22/03/2022

SUBJECT CODE – 21ELH-101

1. Aim: To design simple DC motor control circuit.

2.Apparatus: ARDUINO UNO, DC motor, L293D, connecting wires.
potentiometer.

3.Circuit Diagram:

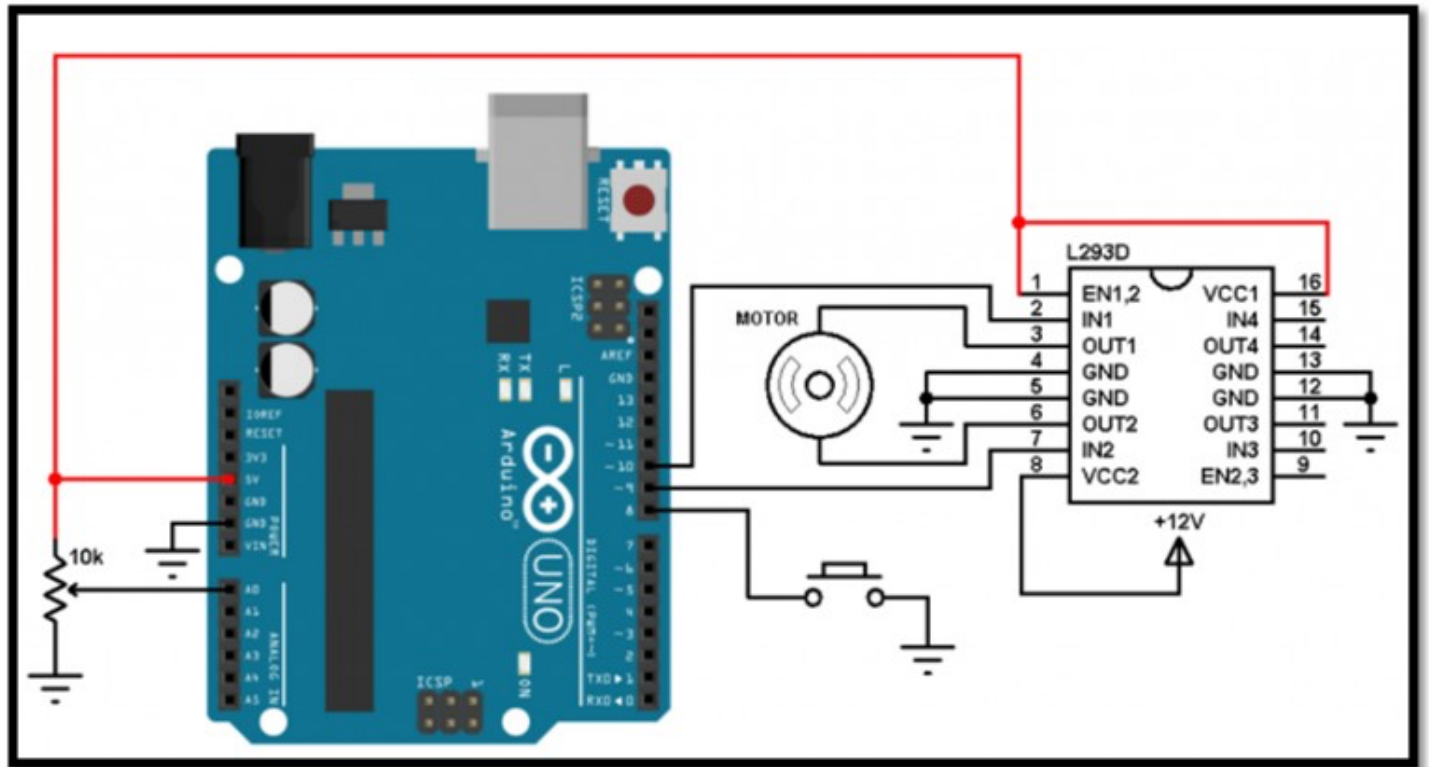


Fig.1 DC Motor Circuit

4.Program:

```
#define button 8
```

```
#define pot 0
```

```
#define pwm1 9
```

```
#define pwm2 10
```

```
boolean motor_dir = 0;
```

```
int motor_speed;
```

```
void setup() {
```

```
  pinMode(button, INPUT_PULLUP);
```

```
  pinMode(pwm1, OUTPUT);
```

```
  pinMode(pwm2, OUTPUT);
```

```
}

void loop() {
  motor_speed = analogRead(pot) / 4;
  if(motor_dir)
    analogWrite(pwm1, motor_speed);
  else
    analogWrite(pwm2, motor_speed);
  if(!digitalRead(button)){      // If direction button is pressed
    while(!digitalRead(button));  // Wait until direction button released
    motor_dir = !motor_dir;       // Toggle direction variable
    if(motor_dir)
      digitalWrite(pwm2, 0);
    else
      digitalWrite(pwm1, 0);
  }
}
```


5.Tinker Cad Result:

Browser tabs: (3) This Episode is full of EPIC, Content, Circuit design Epic KrunK-Migelo

URL: tinkercad.com/things/hEzNRV4HGE1-epic-krunk-migelo/editel

User: Epic KrunK-Migelo

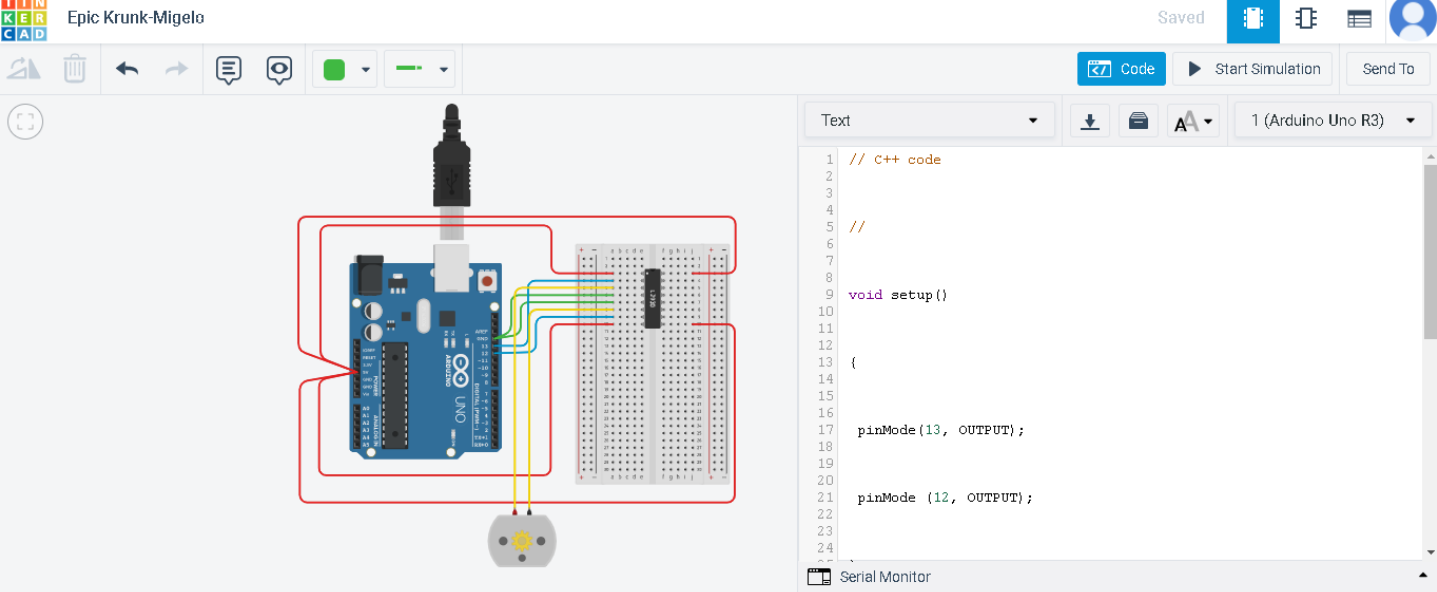Buttons: Saved, Start Simulation, Send To



```
1 // C++ code
2
3
4
5 //
6
7
8
9 void setup()
10
11
12 {
13
14
15
16
17   pinMode(13, OUTPUT);
18
19
20
21   pinMode (12, OUTPUT);
22
23
24
```

Serial Monitor

File: dc motor circuit.jpg

Windows taskbar: 9:00 PM 3/22/2022


Browser tabs: (3) This Episode is full of EPIC, Content, Circuit design Epic KrunK-Migelo

URL: tinkercad.com/things/hEzNRV4HGE1-epic-krunk-migelo/editel

User: Epic KrunK-Migelo

Buttons: Saved, Stop Simulation, Send To

Simulator time: 00:00:10

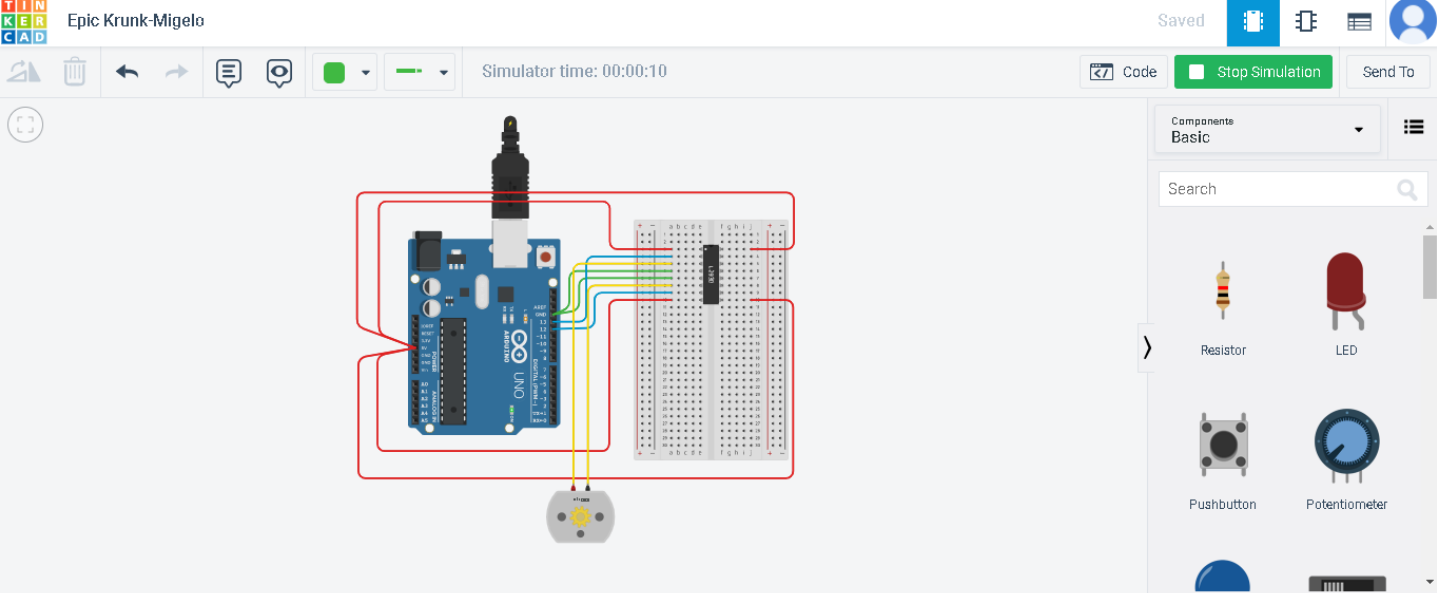


Components Basic

Search


- Resistor
- LED
- Pushbutton
- Potentiometer

File: dc motor circuit.jpg

Windows taskbar: 9:00 PM 3/22/2022

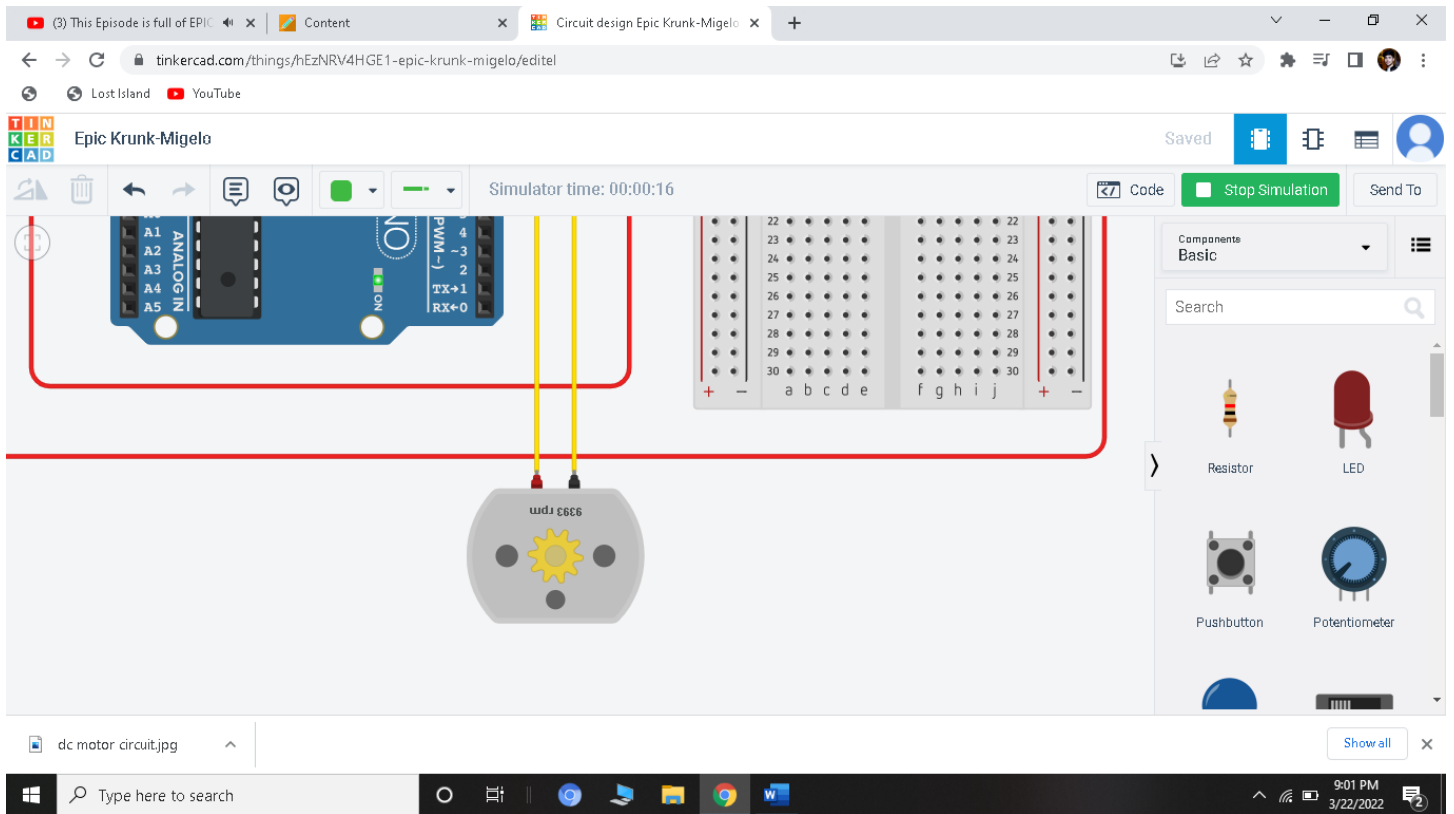

When 13 is High; 12 is Low

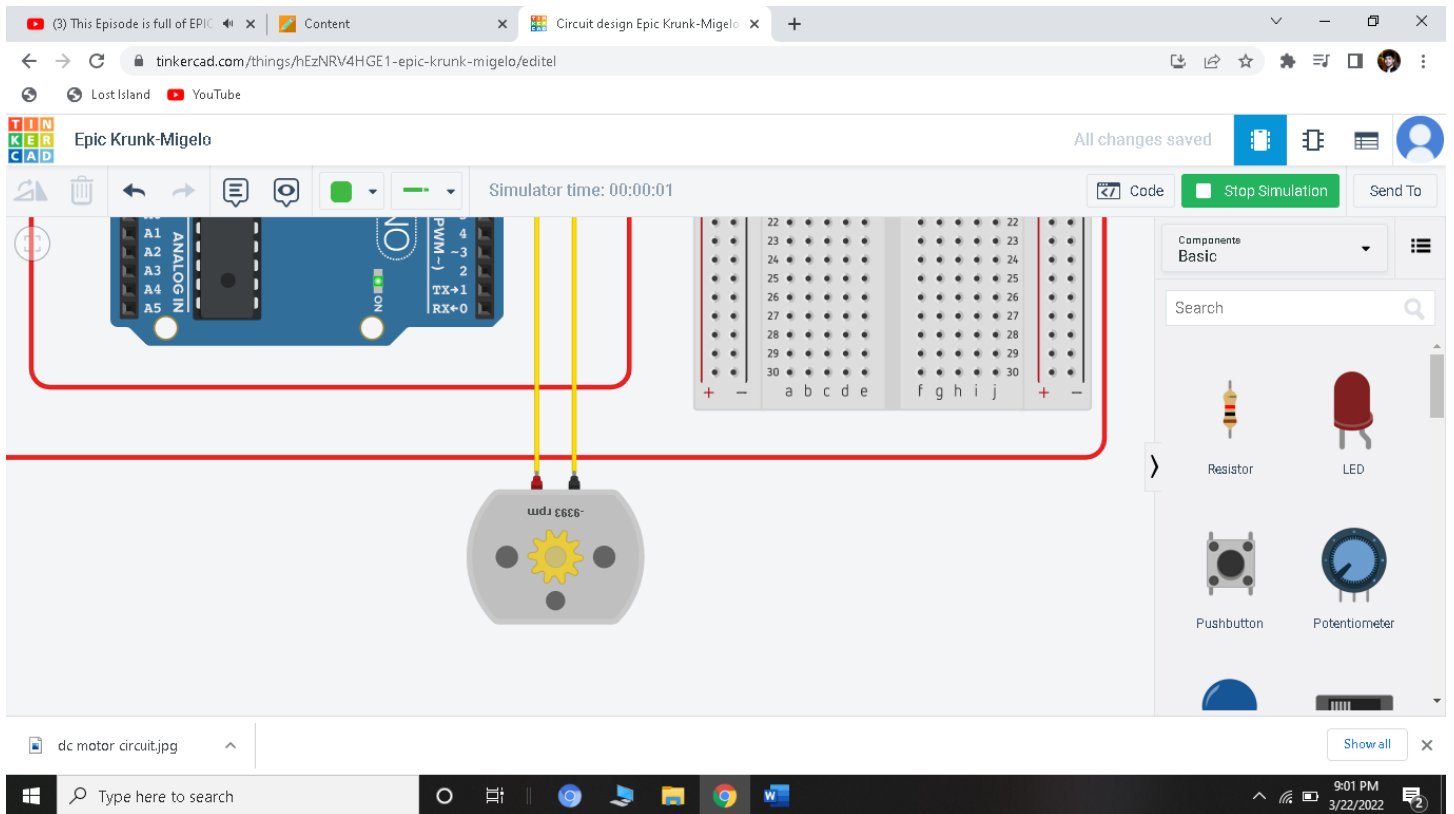

When 12 is High; 13 is Low

6.Result: Designing of simple DC motor control circuit using Arduino is verified after uploading the program.

THANK YOU